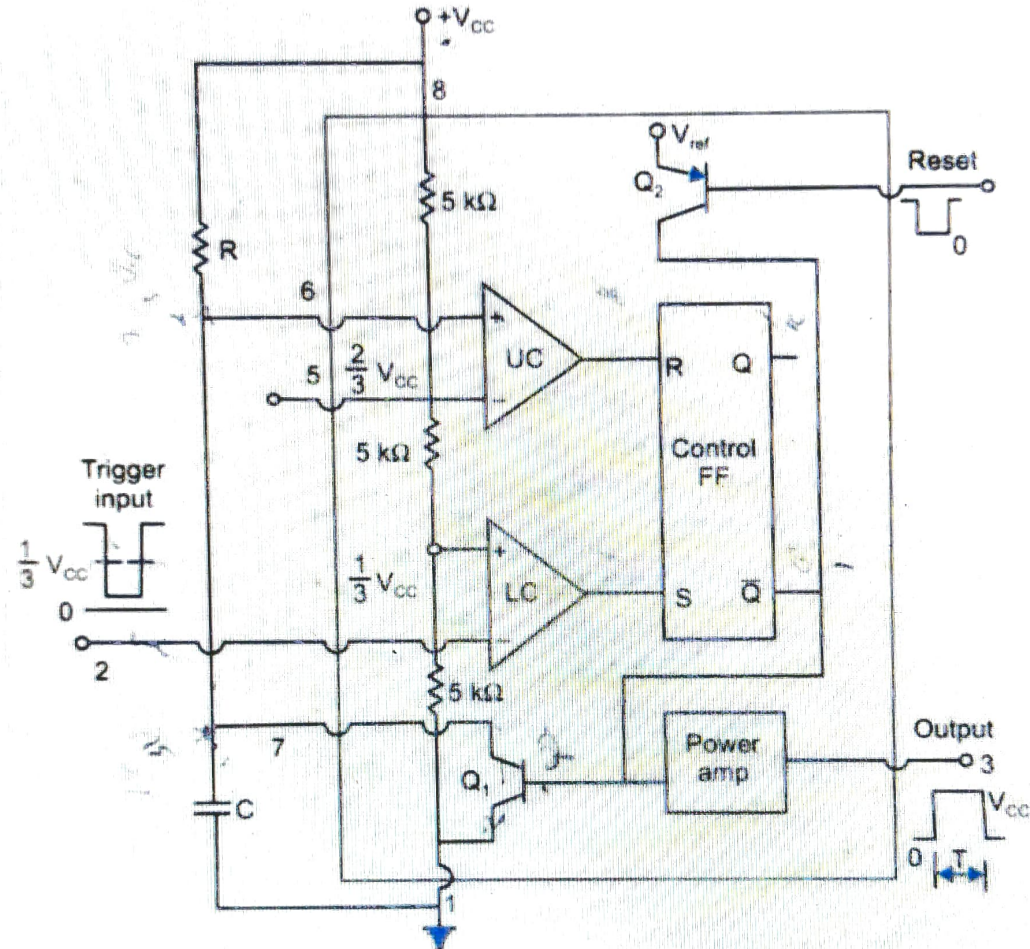


Functional diagram of Monostable operation of 555



Pulse Width Calculation

The voltage across the capacitor is,

$$v_c = V_f + (V_i - V_f)e^{-t/R_1C_1}$$

$V_f = +V_{CC}$, $V_i = 0V$, and the capacitor is charging to

$$\frac{2}{3}V_{CC} = V_{CC} - V_{CC}e^{-t/R_1C_1}$$

$$\frac{2}{3} = 1 - e^{-t/R_1C_1}$$




$$-t/R_1C_1 = \ln\left(\frac{1}{3}\right) = -1.098$$

$$e^{-t/R_1C_1} = 1$$

$$t = 1.1$$

$$T = 1.1 R_a C$$

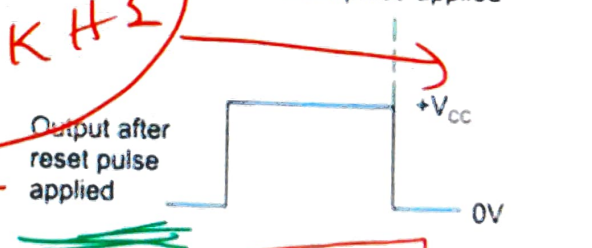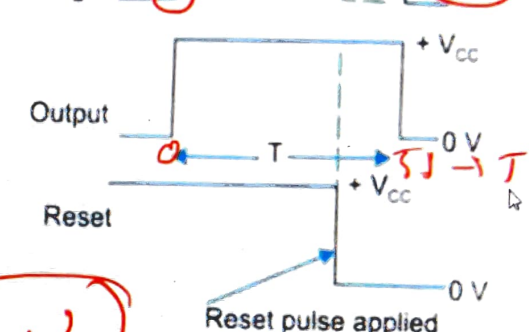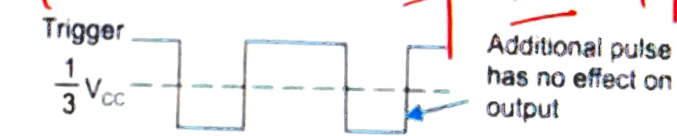Handwritten notes: 1mH , $C = 1\text{nF}$, $R_a = 1\text{K}\Omega$, $T \approx 1\mu\text{s}$





$$f = \frac{1}{T}$$

$$= 1\text{MHz}$$



- The 555 can operate as
 - Mono/bi-stable
 - Astable modedepending on the external components
- It produce
 - a single pulse when triggered, or
 - it can produce a continuous pulse train as long as it remains powered.



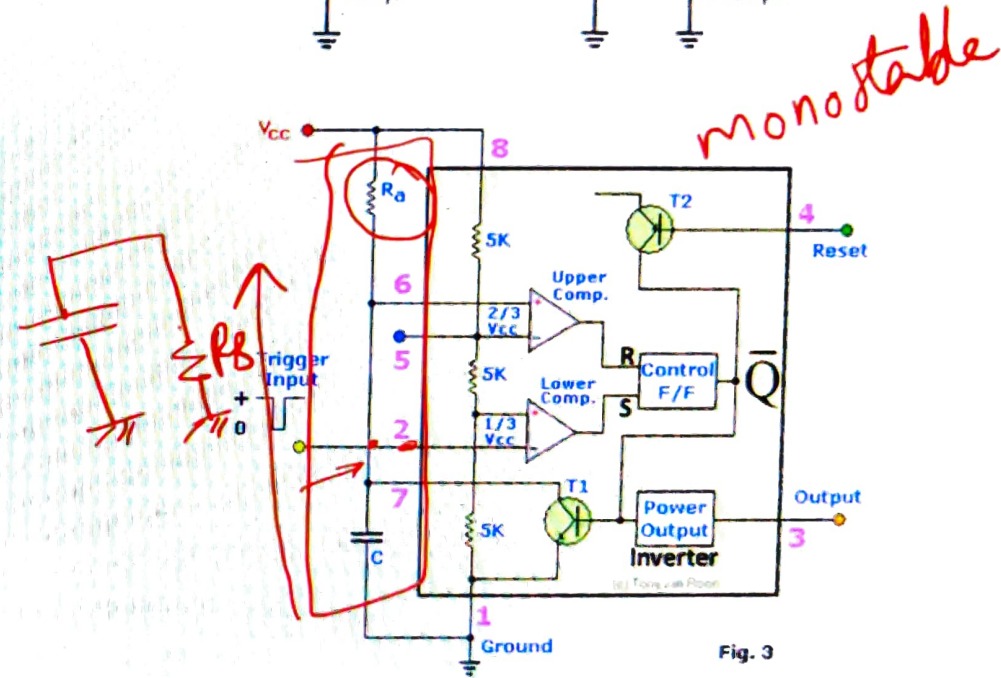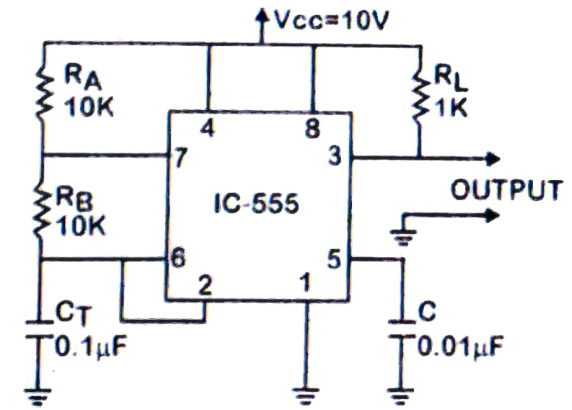- The key external component of the astable timer is the capacitor
- The astable function is achieved by charging/discharging a capacitor through resistors connected, respectively, either to V_{CC} or GND.




Astable multivibrator

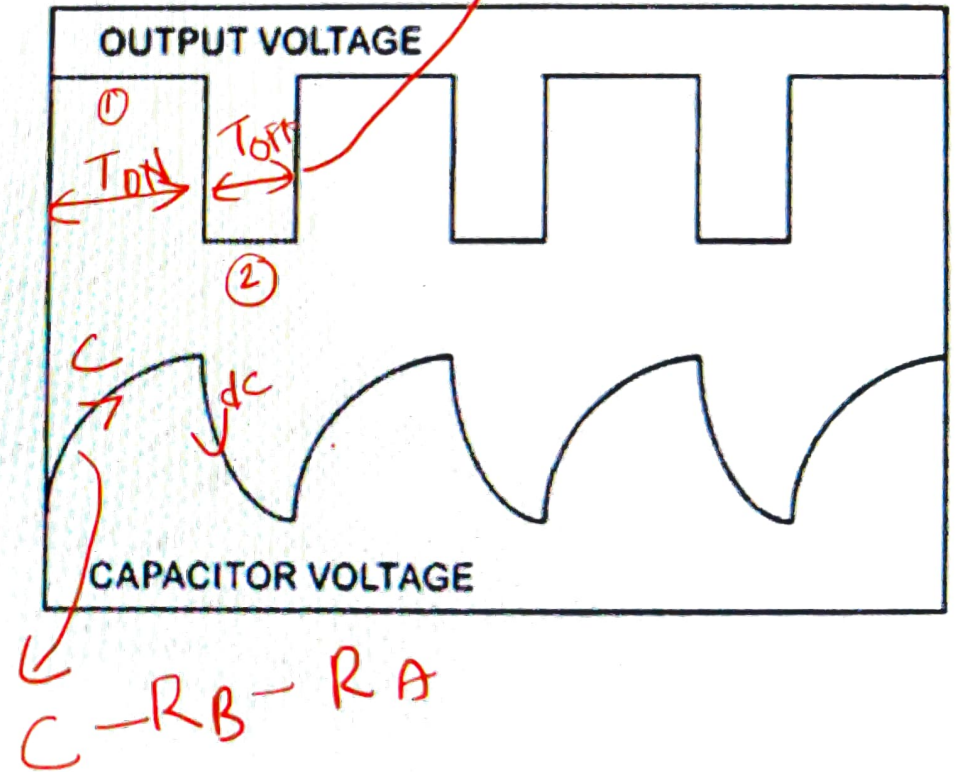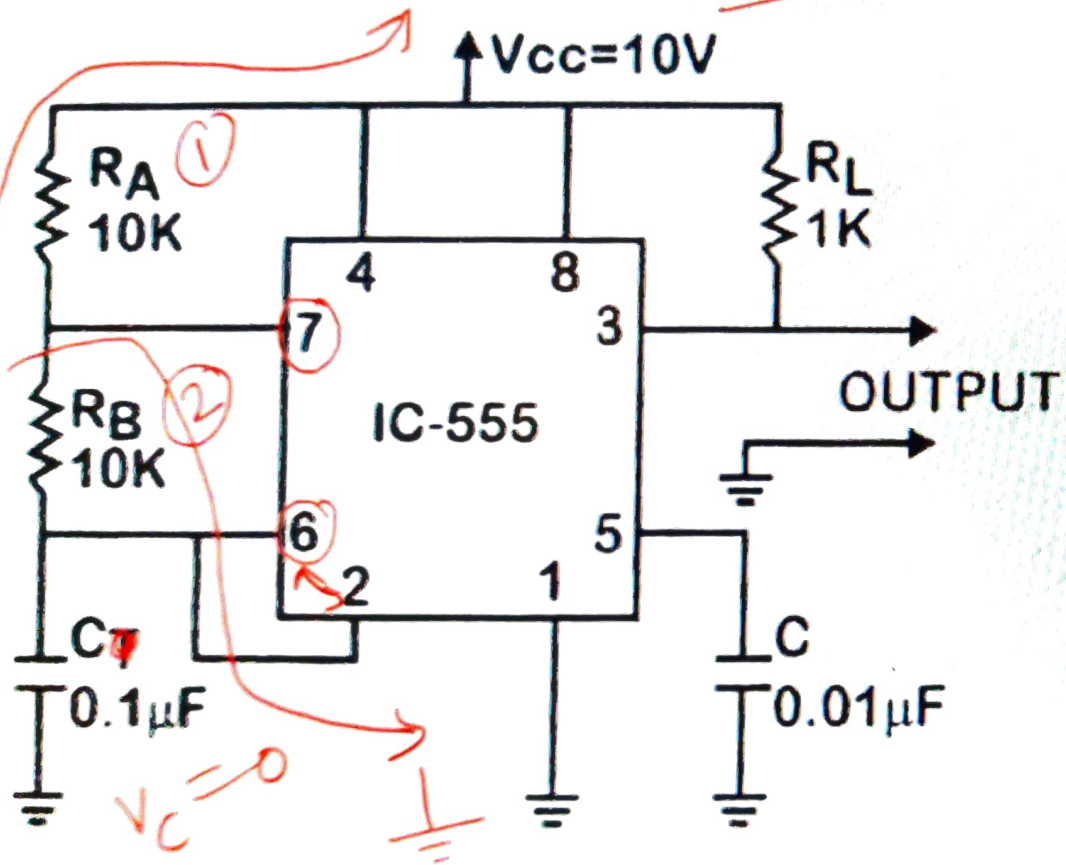

Rectangular waveform

$$\delta = \frac{\tau}{T} \times 100\%$$

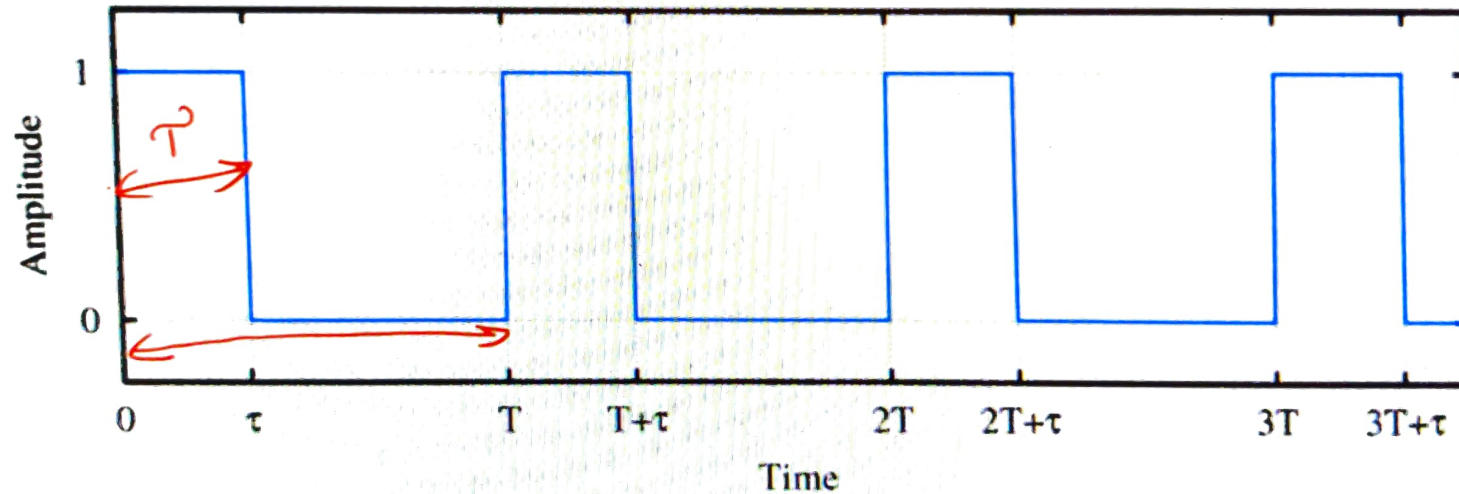- Referring to the above figure of a rectangular waveform, the time period of the pulse is defined as T and duration of the pulse (ON time) is τ .
- Duty cycle can be defined as the On time/Period that is, τ/T in the above figure. Obviously, a duty cycle of 50% will yield a square wave.





$$\frac{1}{3} V_{CC} \rightarrow \frac{2}{3} V_{CC}$$

$$T = T_{ON} + T_{OFF}$$

$$\delta = \frac{T_{ON}}{T} \times 100$$

The time for charging C from $\frac{1}{3}$ to $\frac{2}{3} V_{CC}$, i.e, **ON Time** = $0.693 (R_A + R_B) \cdot C$

The time for discharging C from $\frac{2}{3}$ to $\frac{1}{3} V_{CC}$, i.e. **OFF Time** = $0.693 R_B \cdot C$

To get the total oscillation period, just add the two: T_{OFF} \rightarrow

$$T_{osc} = 0.693 \cdot (R_A + R_B) \cdot C + 0.693 \cdot (R_B) \cdot C = 0.693 \cdot (R_A + 2 \cdot R_B) \cdot C$$

Thus,

$$f = \frac{1.44}{(R_A + 2R_B) \cdot C}$$

$$f_{osc} = 1/T_{osc} = 1.44 / (R_A + 2 \cdot R_B) \cdot C$$


$$\text{Duty cycle} = \frac{R_A + R_B}{R_A + 2 \cdot R_B}$$

$$\delta = \frac{R_A + R_B}{R_A + 2R_B}$$

Astable MV

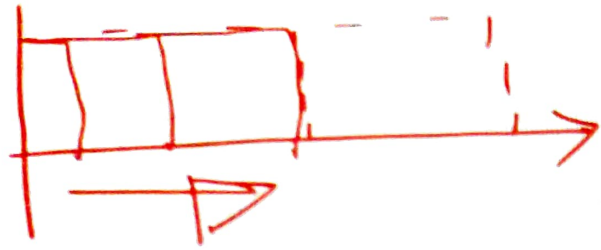- $R1 = 1\text{ k}\Omega$, $R2 = 2\text{ k}\Omega$, $C = 10\text{ }\mu\text{F}$.
- Calculate duty cycle
- Frequency \rightarrow .






Astable MV

• $R1 = 1k, R2 = 2k, C = 10 \mu F$.

• Calculate duty cycle $\rightarrow 8$

• Frequency $\rightarrow f$

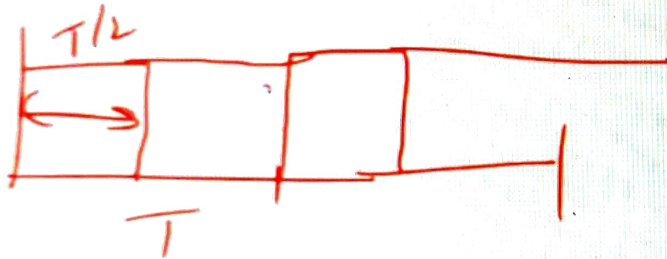

SCR



$$T_{on} =$$

$$T_{off} =$$

$$8 =$$

$$f =$$

