
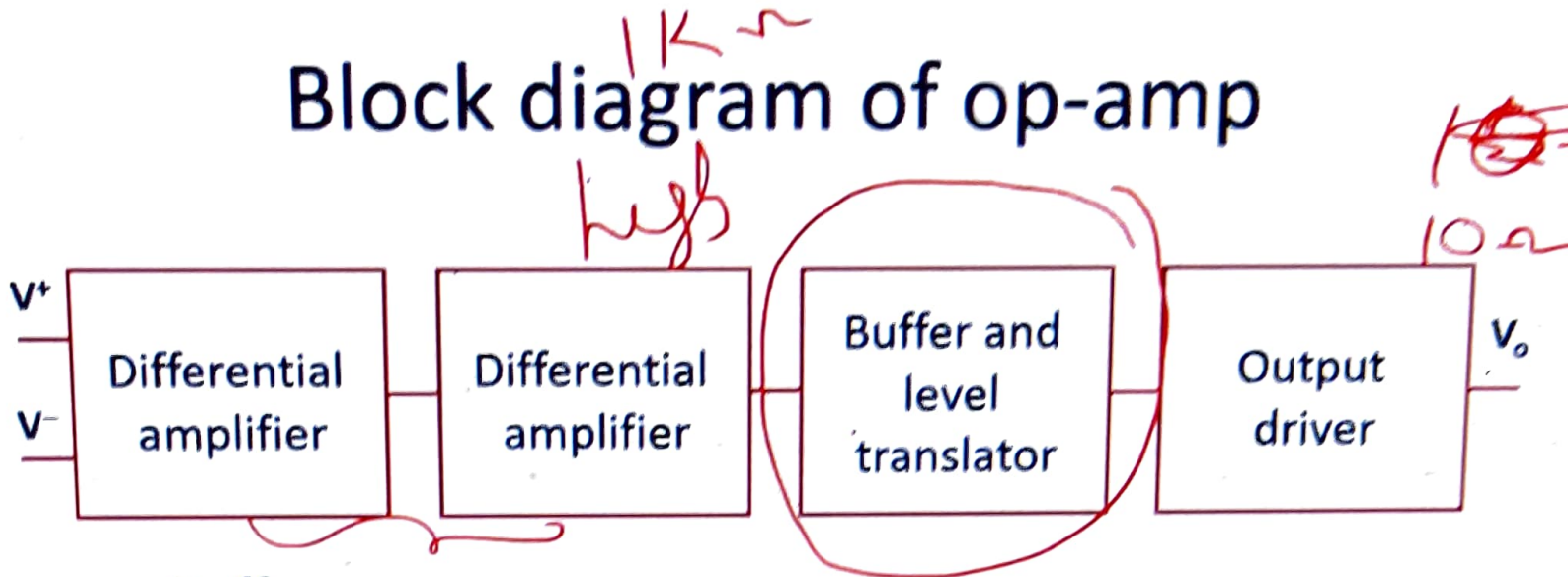


Block diagram of op-amp

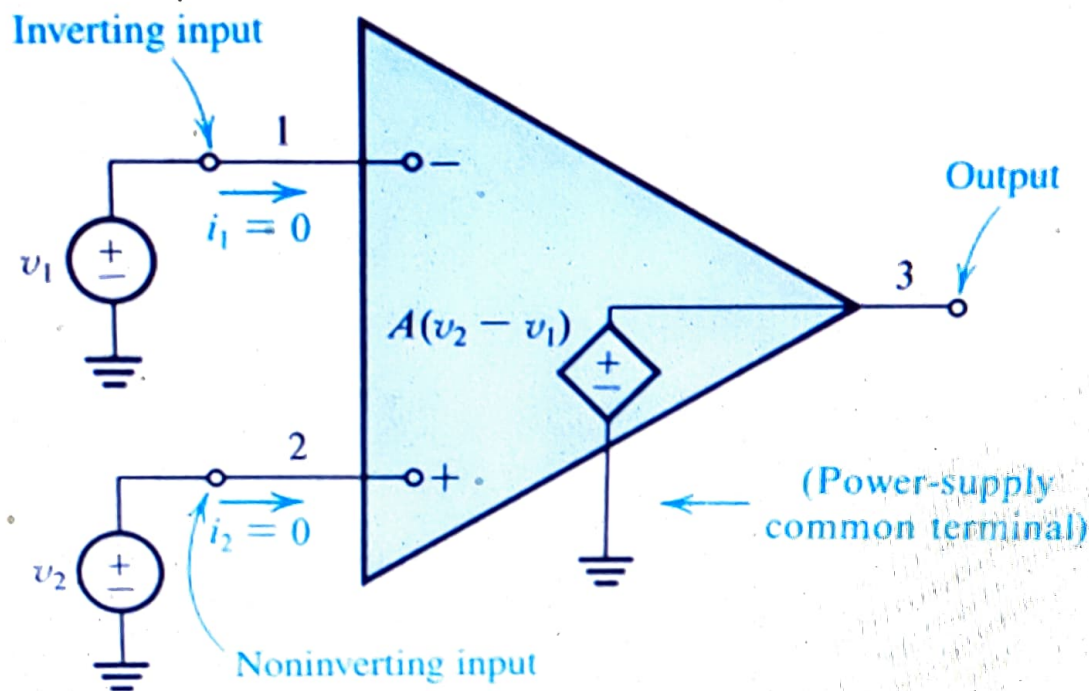

- Buffer
 - Emitter follower
 - Very high input impedance, to prevent loading to the amplifier
- Level shifter
 - Adjusts DC voltages so that output voltage is zero for zero input voltage


Equivalent circuit of the ideal op-amp (VCVS model of op-amp)



Operations of op-amp


- **Open loop**

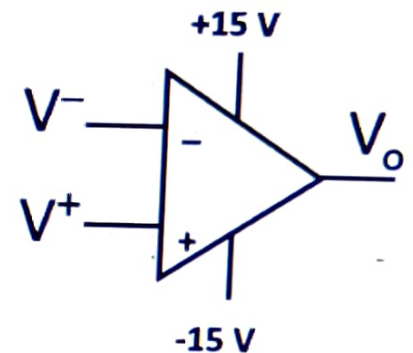- Output is driven into saturation.
- Comparator
- Zero crossing detector



- **Closed loop**

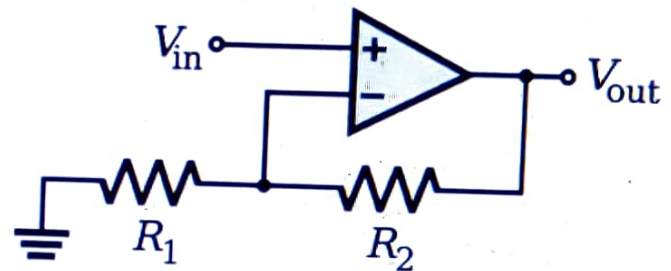
- Negative feed back
- Linear output range



Analysis of op-amp

- Assumptions

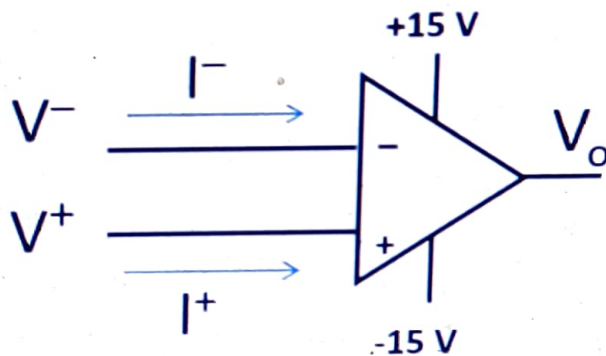
- Current entering the op-amp terminals is zero, $I^+ = I^- = 0$
- Difference voltage is zero, $V^+ - V^- = 0$




Non-inverting op-amp

*negative
feedback*
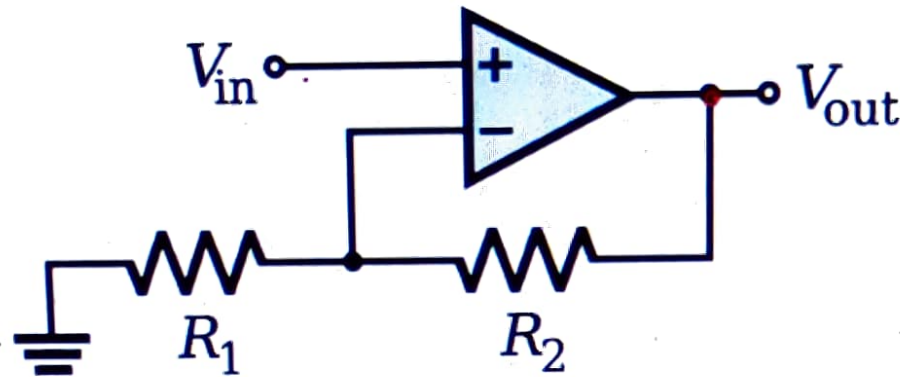
$$i_1 = i_2$$
$$\frac{0 - V_{in}}{R_1} = \frac{V_{in} - V_{out}}{R_2}$$


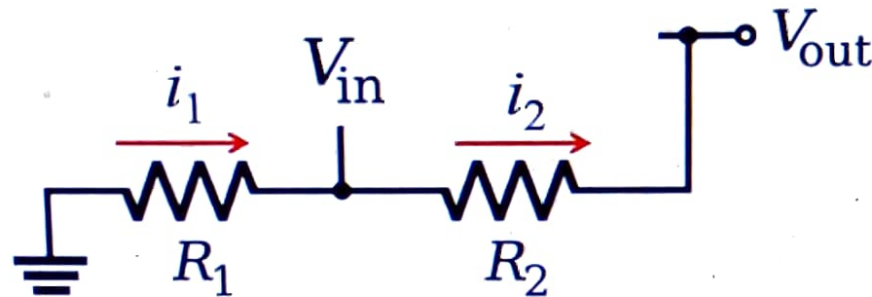
$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$






Non-inverting op-amp

KCL
 $i_1 = i_2$
 $i_1 = 0 + i_2$
 $i_1 = i_2$

$$\frac{0 - V_{in}}{R_1} = \frac{V_{in} - V_{out}}{R_2}$$


$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

$$V_{out} = K V_{in}$$

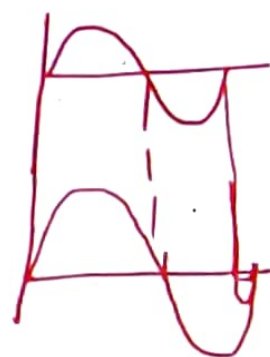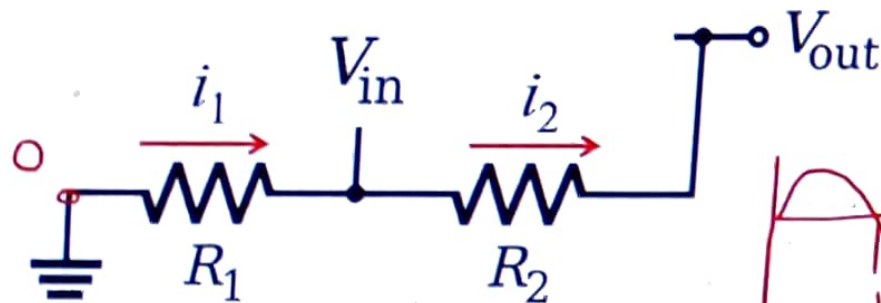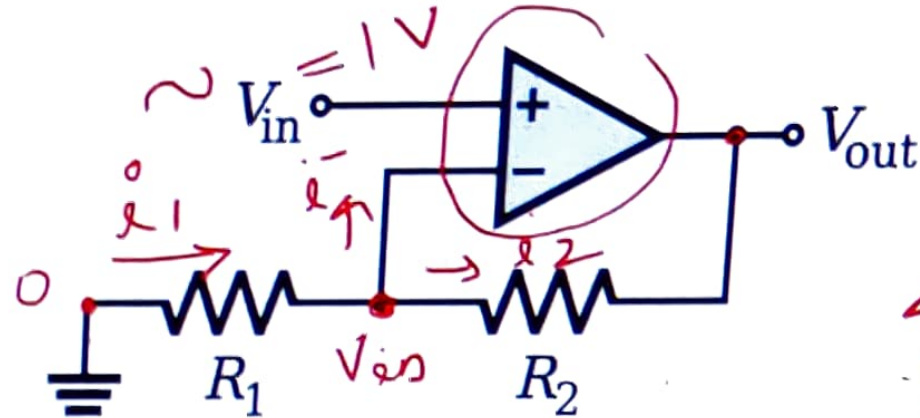


Inverting op-amp

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

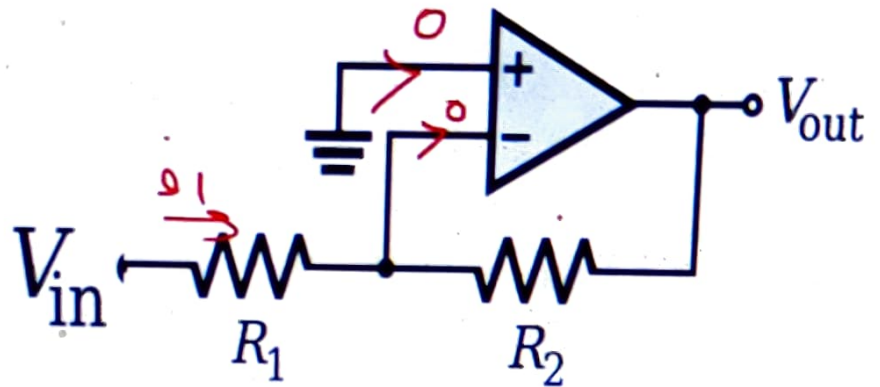


Inverting summing amplifier

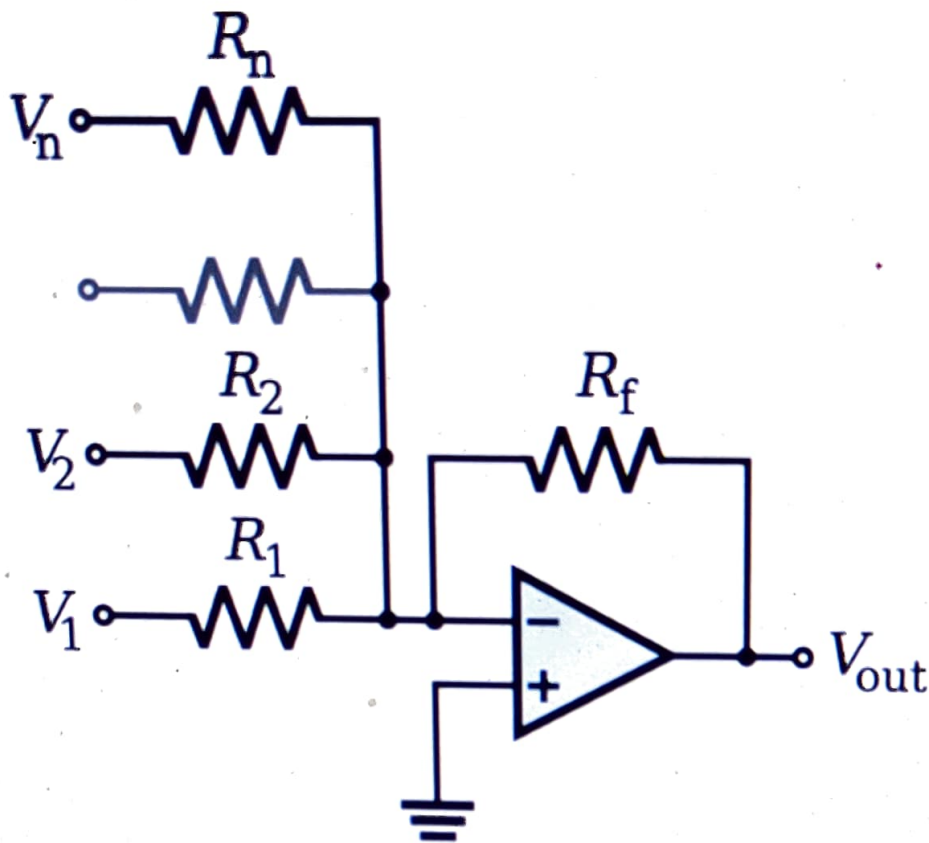

$$V_{out} = - \left(\frac{R_f}{R_1} + \frac{R_f}{R_2} + \dots + \frac{R_f}{R_n} \right) V_{in}$$

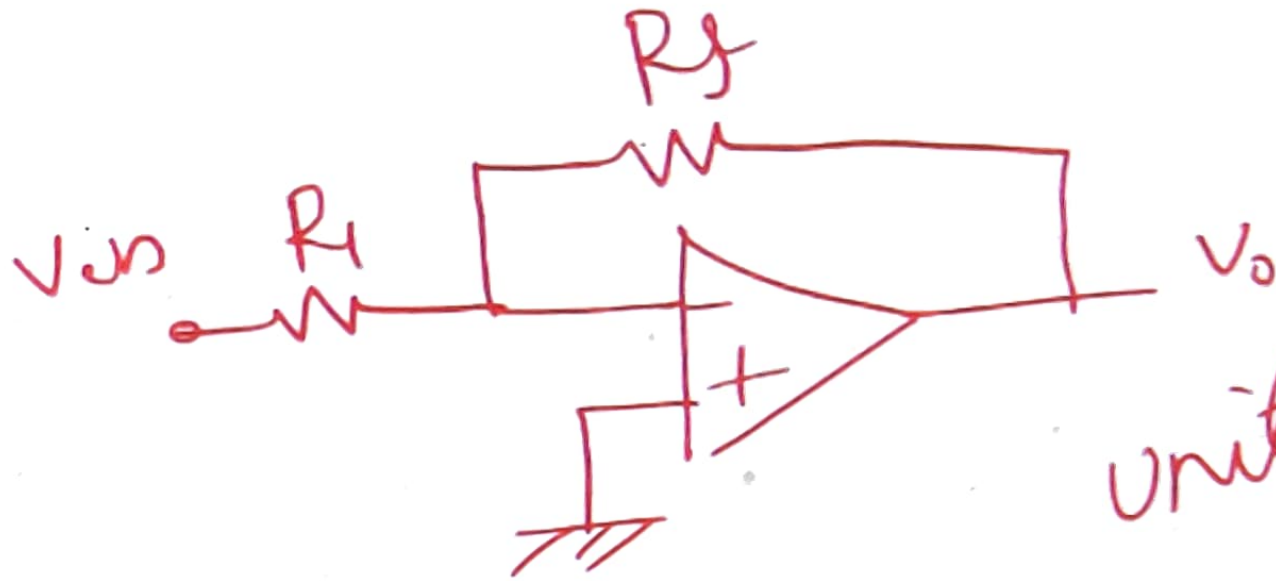Design an inverting op-amp with gain of 1




units gain

$$V_o = - \left(\frac{R_f}{R_i} \right) V_{in}$$

↓ gain = 1

$$\underline{\underline{V_o = - V_{in}}}$$


Difference amplifier

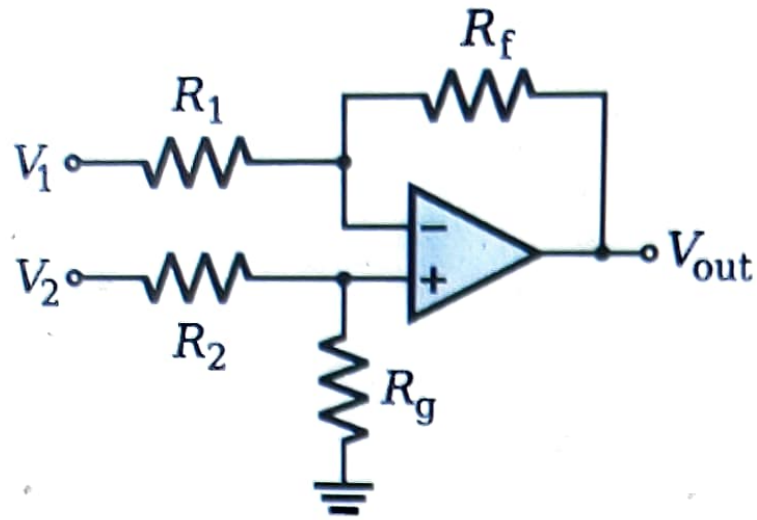

Meeting details ^


Type here to search

Difference amplifier

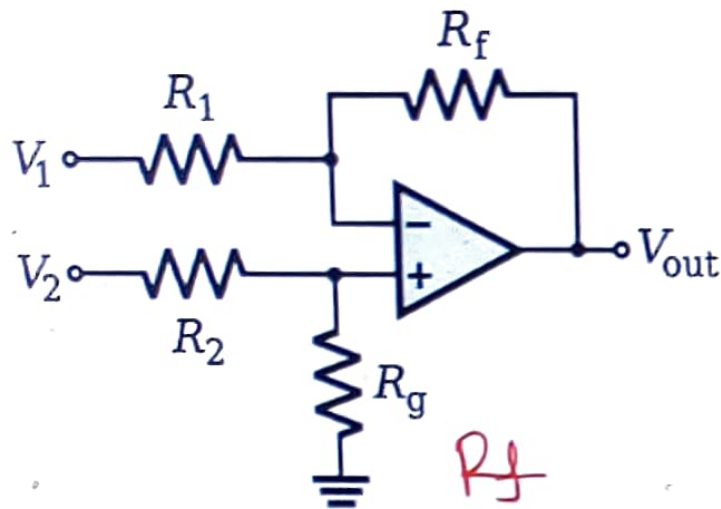

Superposition → take only one source at a time

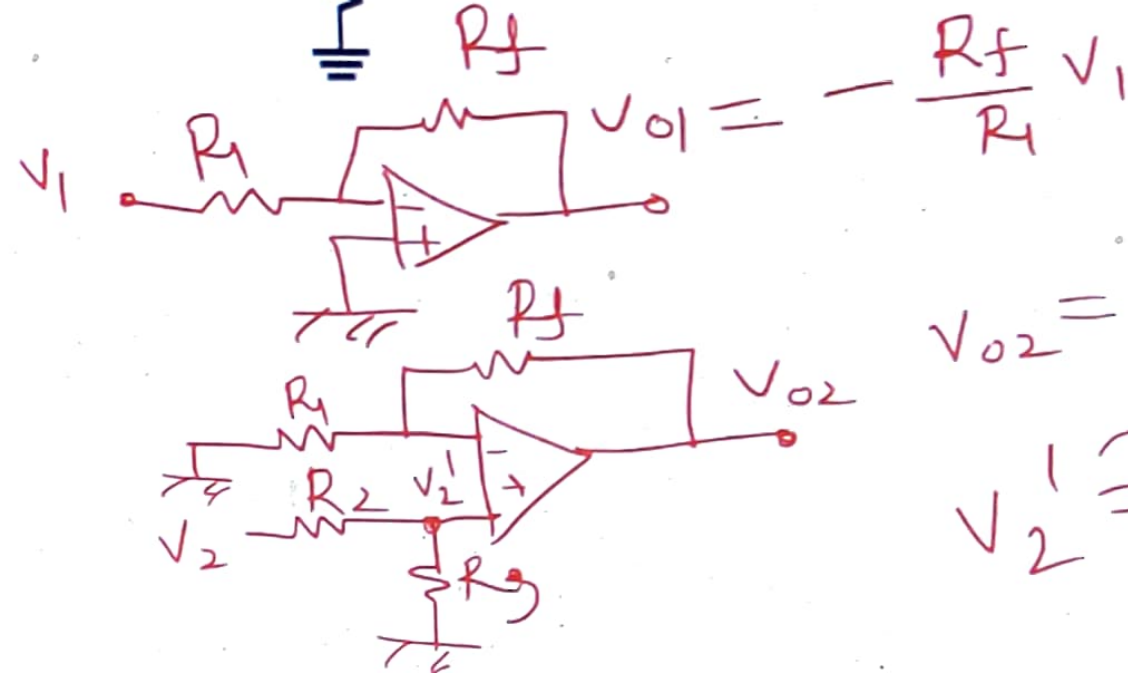① $V_{out} = V_{o1} + V_{o2}$
 $= -[A] + [B]$



$$V_{o2} = \left(1 + \frac{R_f}{R_g}\right) V_2'$$

$$V_2' = \left(\frac{R_g}{R_2 + R_g}\right) V_2$$

