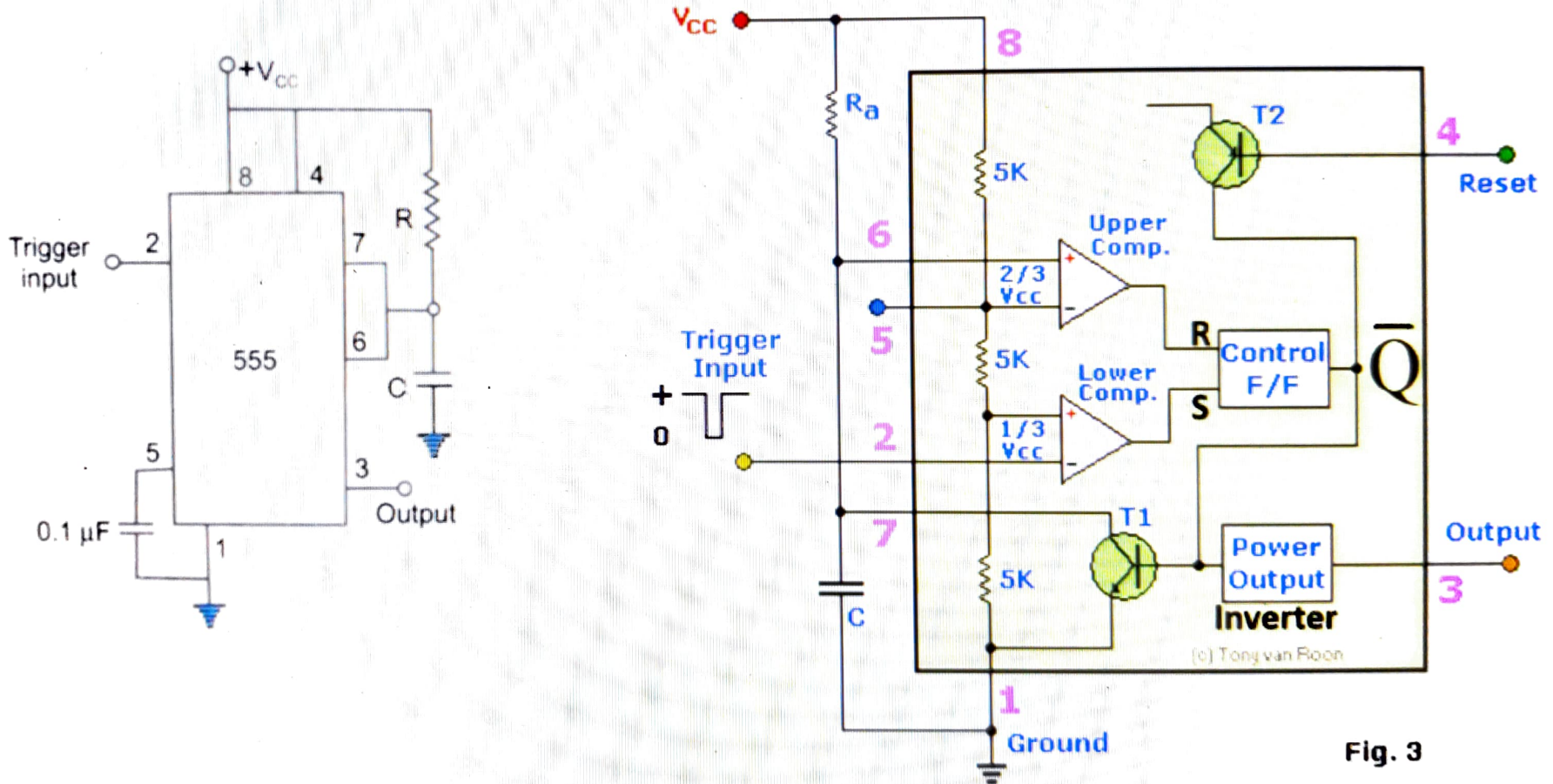


Functional diagram of Monostable operation of 555 timer



Monostable operation of 555 timer

- In the standby state
 - FF is reset, and holds transistor T1 in ON state
 - External capacitor C is short circuited and clamped to ground
 - Output is LOW

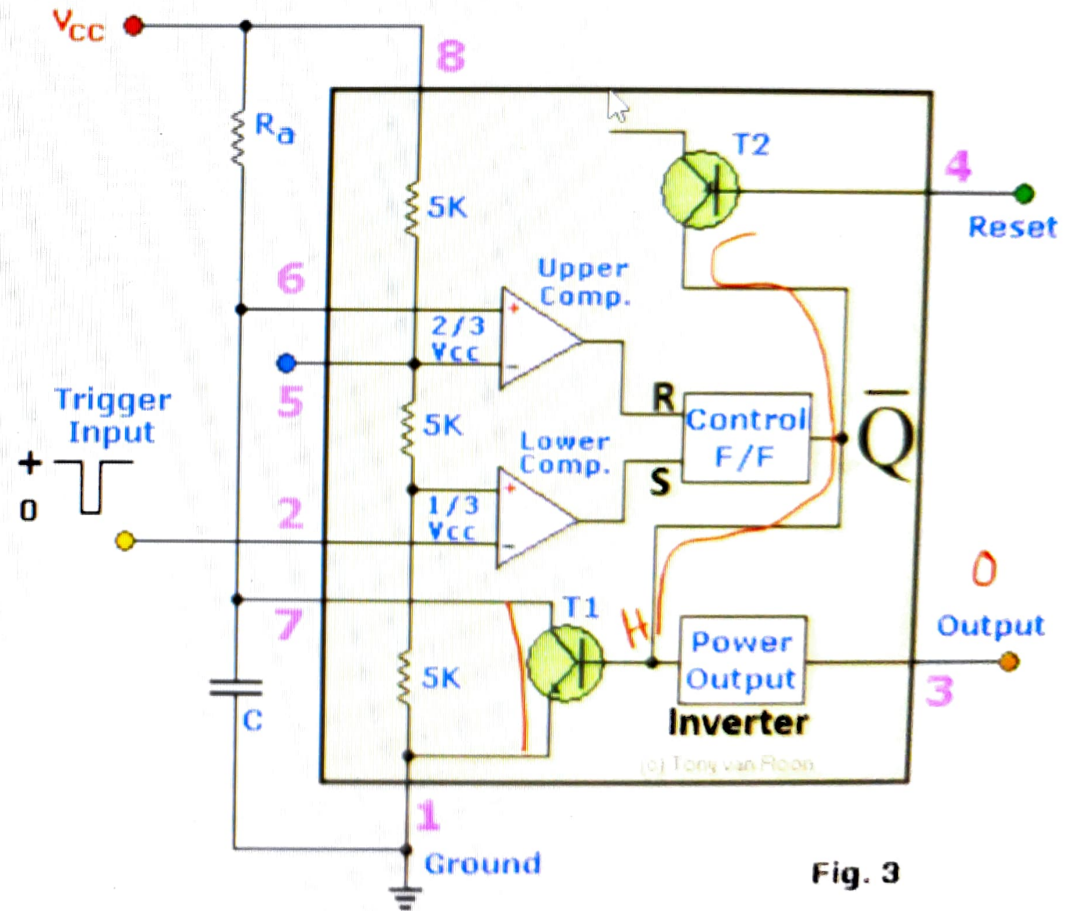


Fig. 3

Monostable operation of 555 timer

- As trigger passes through less than $V_{cc}/3$,
 - FF is set
 - Q is high and \bar{Q} is low
 - Transistor T1 is OFF
 - Output is HIGH
 - C is unclamped, voltage across C rises exponentially through R_a towards V_{cc}
 - Time constant is $R_a C$
 - After a time period (T), the capacitor voltage as it goes beyond $(2/3)V_{cc}$

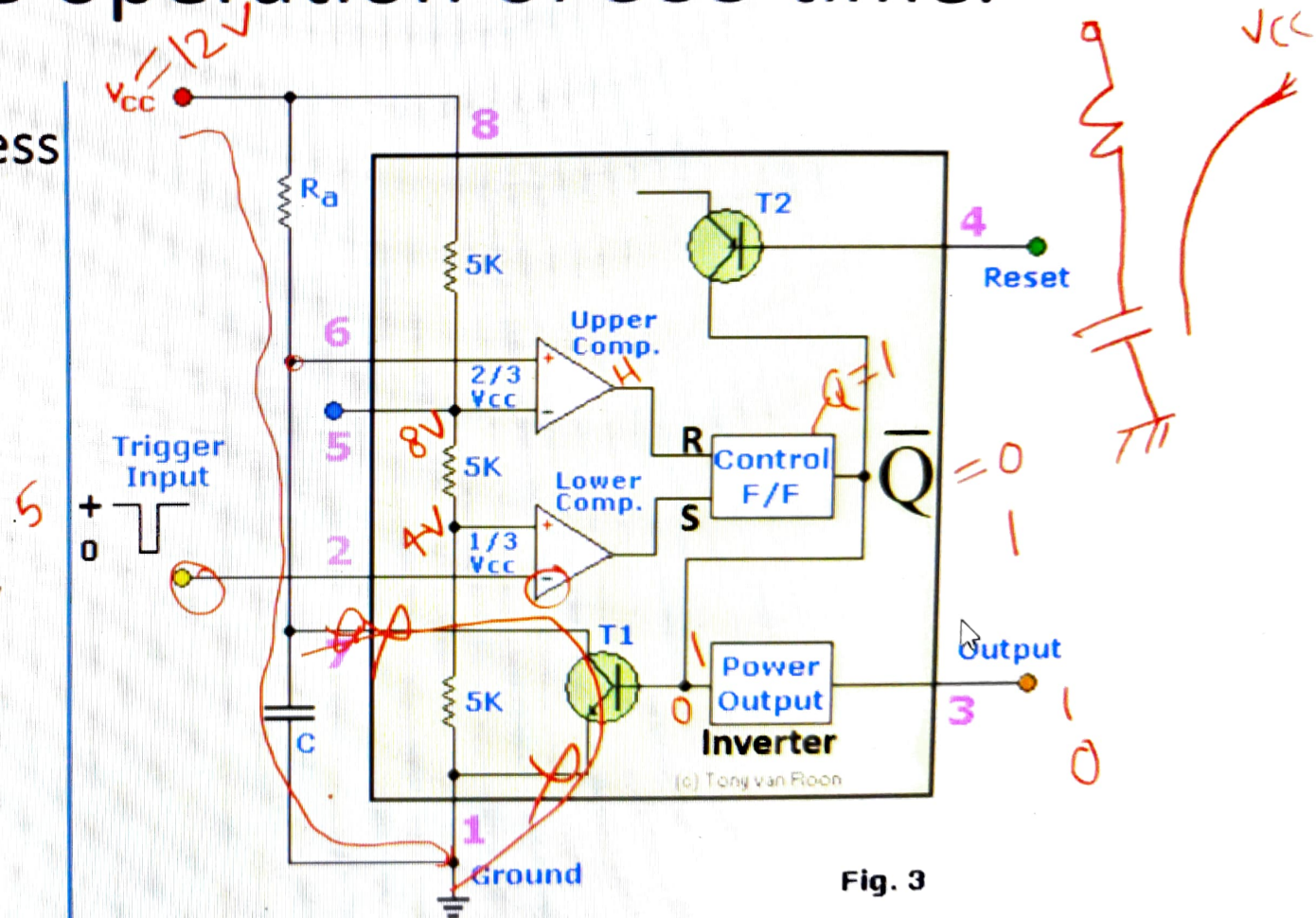



Fig. 3

standby Reset $\rightarrow \bar{Q} \rightarrow H$; $Q \rightarrow L$
 $T1 \rightarrow ON \rightarrow C \rightarrow gnd$

$$V_{TI} = 3.99 \text{ (} V^+ \leftarrow V \text{)}$$

$$V_{O,LC} = +V_{sat} \text{ (High)}$$

Set (FF)

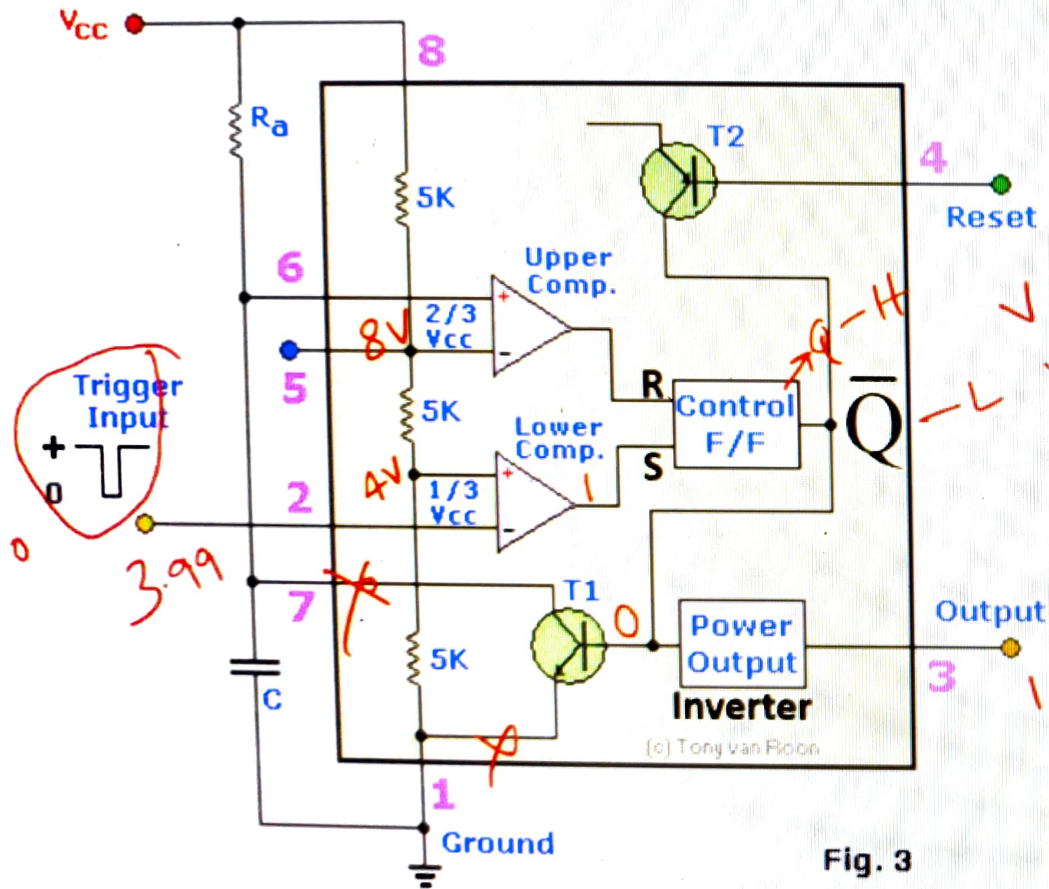

$V_{CC} \rightarrow \Sigma R_a \rightarrow Q \rightarrow 1$
 $\bar{Q} \rightarrow 0$
 e/o $T1 = 0$ $T1$ open
 $C \rightarrow$ unclamped