

Differentiator

$\frac{d}{dt} \rightarrow$ slope

Current flowing through capacitor


$$i_C = C \frac{d}{dt} (v_i - v_N) = C \frac{dv_i}{dt}$$

Nodal equation at N

$$C \frac{dv_i}{dt} + \frac{v_o}{R_F} = 0$$

Solving

$$v_o = -R_F C \frac{dv_i}{dt}$$

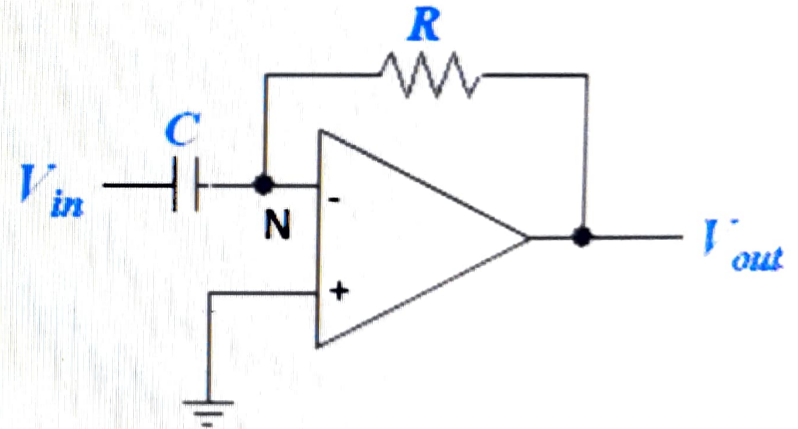

Differentiator

Current flowing through capacitor

$$i_c = C \frac{d}{dt}(v_{in} - v_N) = C \frac{dv_{in}}{dt}$$


Nodal equation at N

$$C \frac{dv_i}{dt} + \frac{v_o}{R_F} = 0$$

Solving

$$v_o = -R_F C \frac{dv_{in}}{dt}$$

$\frac{d}{dt} \rightarrow$ slope

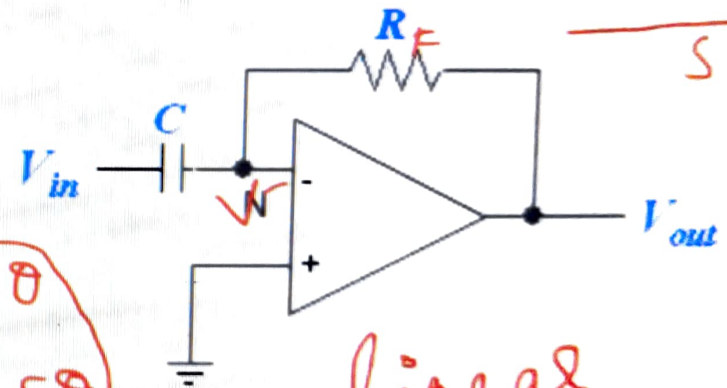

linear

$$V^- = V^+ = 0$$

$$\begin{aligned} v_{in} &= A \sin \theta \\ v_o &= (-A) \cos \theta \end{aligned}$$

The differentiator circuit of Fig. uses $C = 1 \mu\text{F}$ and $R = 1 \text{ M}\Omega$. In addition to the required input voltage, a noise signal due to mains 'hum' also appears at the input. If the input noise signal $v_n = 5 \sin 314t \text{ mV}$, determine the resulting noise signal at the output.

A

$$CR = 10^{-6} \times 10^6 = 1 \text{ s}$$

$$\text{output noise, } V_{on} = -CR \frac{d}{dt} (5 \sin 314\omega t) \text{ mV}$$

$$= 5 \times 314 \cos 314t \text{ mV}$$

$$V_{on} = 1.57 \cos 314t \text{ V Ans}$$



$$v_o = -RC \frac{dv_{in}}{dt}$$

noise 5 mV
1.57 V

Integrator


Nodal equation at N

$$\frac{v_i}{R_1} + C_F \frac{dv_o}{dt} = 0$$

$$\frac{dv_o}{dt} = -\frac{1}{R_1 C_F} v_i$$

Integrating on both sides
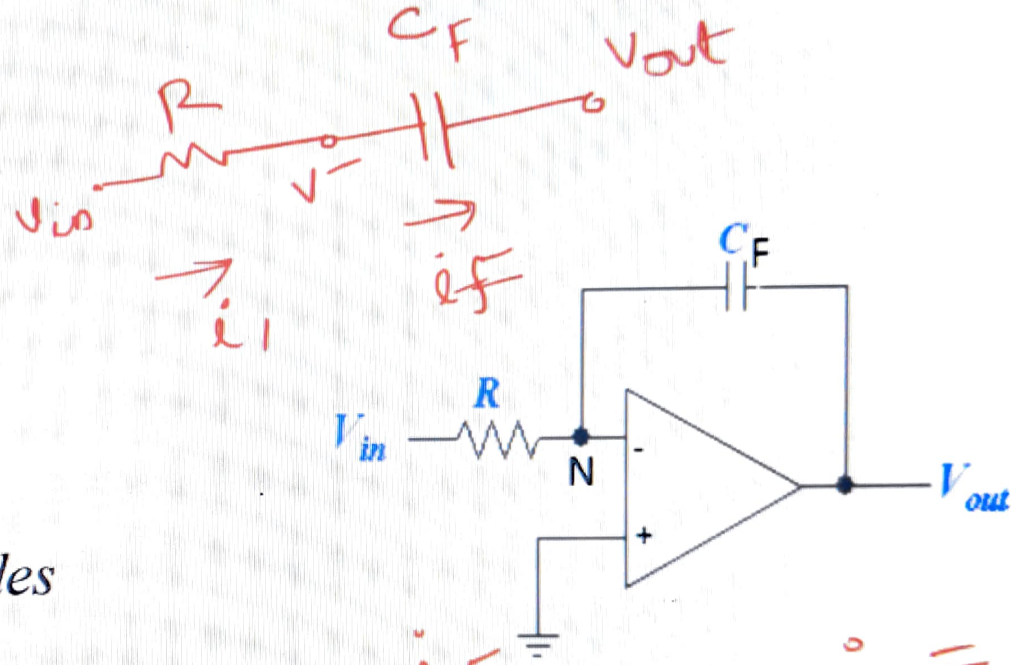
$$v_o = -\frac{1}{R_1 C_F} \int_0^t v_i(t) dt$$



$$i_1 = i_F$$

$$i_1 = \frac{V_{in} - 0}{R}$$

$$i_F = C_F \frac{d(V_{in} - V_o)}{dt}$$

$$= -C_F \frac{dV_o}{dt}$$

Q An integrator circuit is shown in Fig. 11. For this circuit determine the output voltage when $V_i = 25 \sin(314t)$ volt.

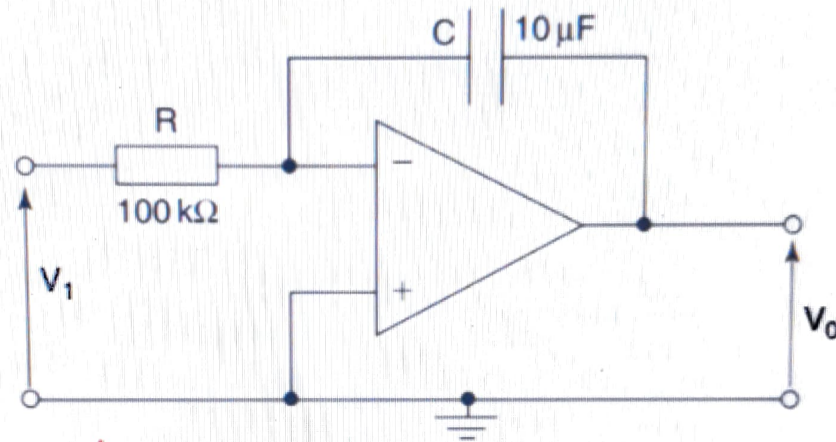


Fig. 11

A


$$\begin{aligned}
 V_o &= \frac{-1}{CR} \int V_i \, dt \text{ volt} \\
 &= \frac{-1}{10^{-5} \times 10^5} \int 25 \sin(314t) \, dt \\
 &= \frac{-1}{314} (-25 \cos 314t)
 \end{aligned}$$

$$V_o = 79.6 \cos(314t) \text{ mV Ans}$$

Assignment B.2

- $R_1 = 10 \text{ k}\Omega$, $R_f = 100 \text{ k}\Omega$, $v_i = 1 \text{ V}$. A load of $25 \text{ k}\Omega$ is connected to the output terminal. Calculate (1) i_1 (2) v_o (3) i_L and (4) total current i_o into the output pin.

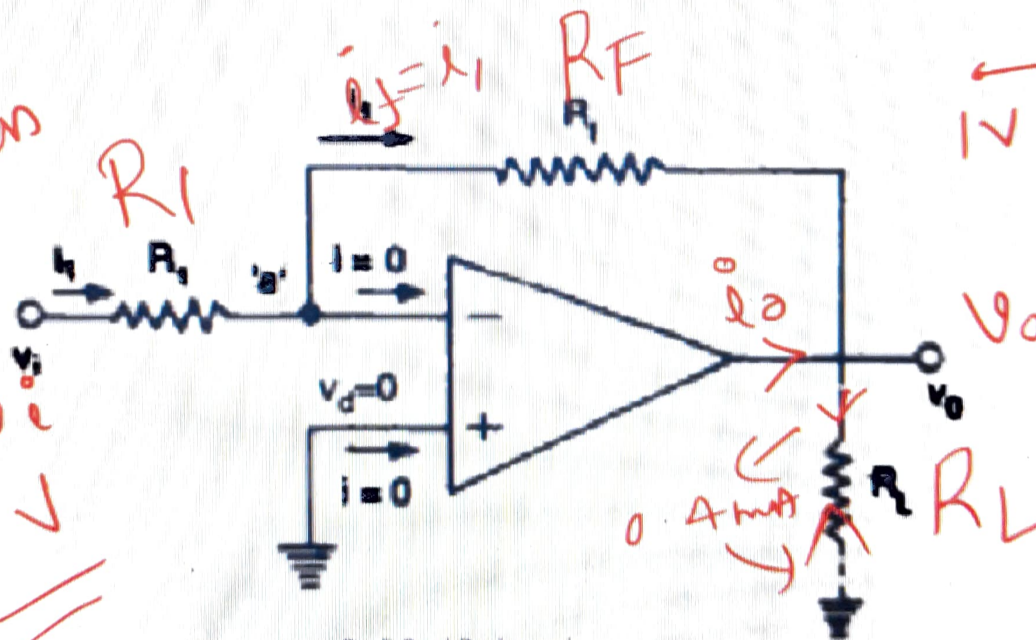
inverting
 $v_o = -\left(\frac{R_f}{R_1}\right)v_{in}$
 $= -10 v_{in} v_i$
 $= -10 \text{ V}$




1 V 10 k 0 V
 $i_1 = \frac{1-0}{10 \text{ k}}$
 $= 0.1 \text{ mA}$
 $i_L = \frac{v_o}{R_L} = -0.4 \text{ mA}$

Assignment B.1


(1)

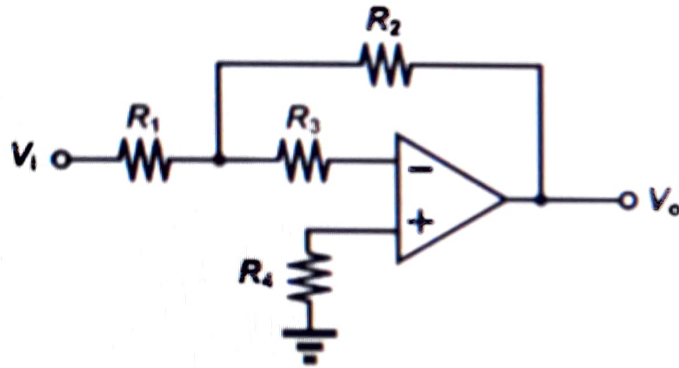

(2)

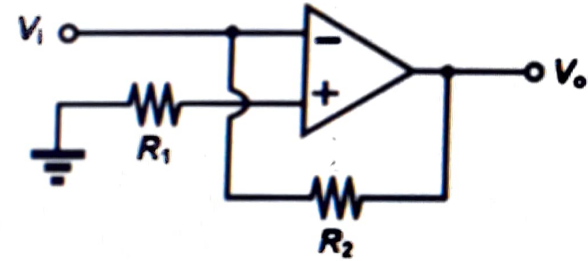


(3)

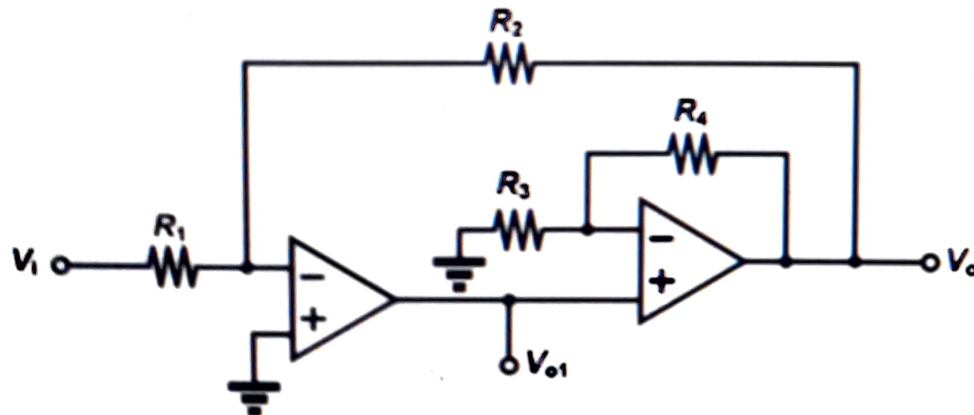

Assignment B.1


(4)

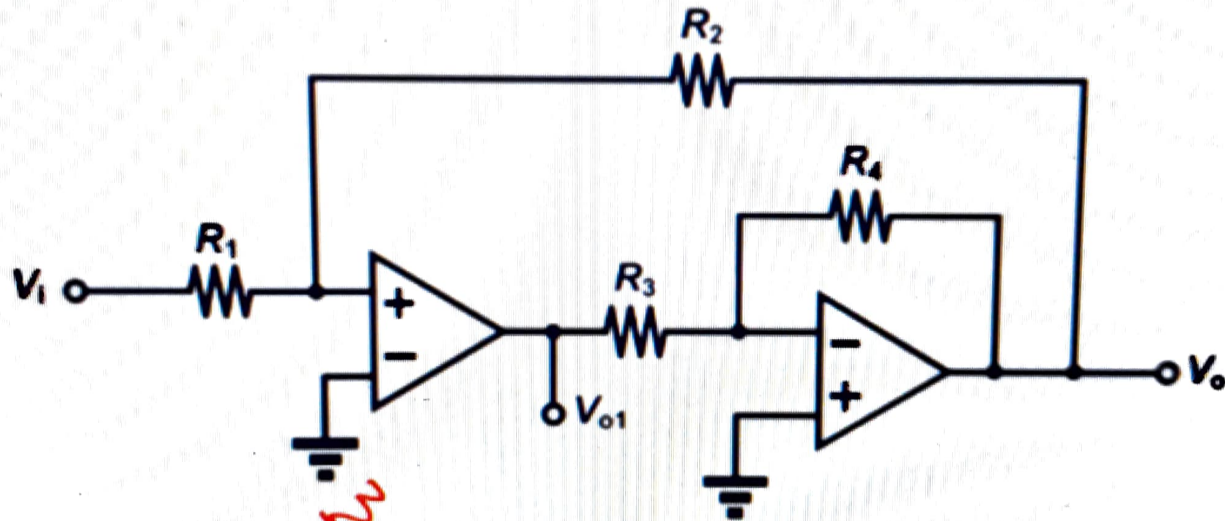

non-uv

The circuit of Fig. has the following combination of inputs and resistors applied. In each case calculate the resulting output voltage.

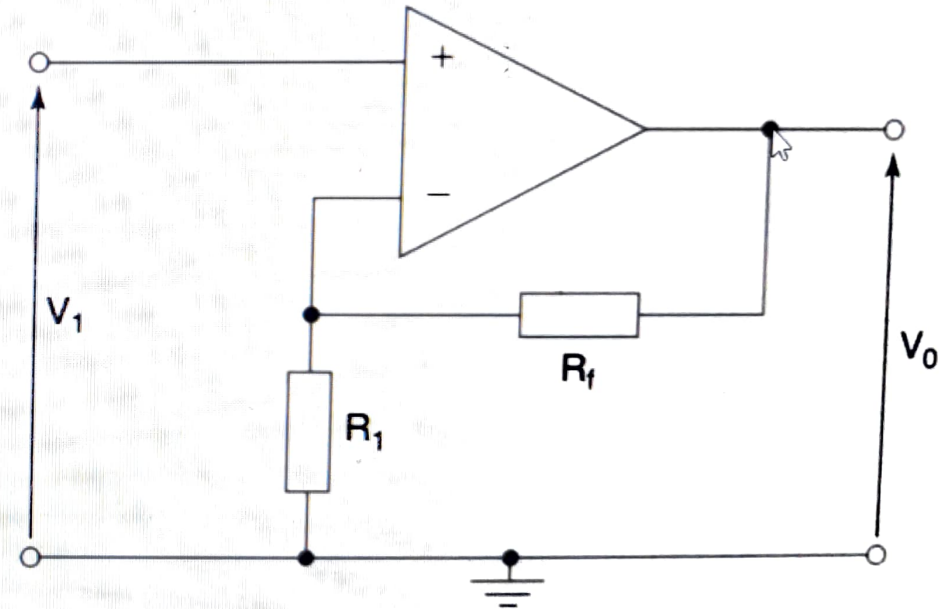
- (a) $R_f = 1\text{ M}\Omega$; $R_1 = 100\text{ k}\Omega$; $V_1 = 0.6\text{ V}$
- (b) $R_f = 100\text{ k}\Omega$; $R_1 = 1\text{ M}\Omega$; $V_1 = -1.5\text{ V}$
- (c) $R_f = 100\text{ k}\Omega$; $R_1 = 1\text{ M}\Omega$; $V_1 = 5 \sin \omega t \text{ volt}$



The circuit of Fig. has the following combination of inputs and resistors applied. In each case calculate the resulting output voltage.


- (a) $R_f = 1 \text{ M}\Omega$; $R_1 = 100 \text{ k}\Omega$; $V_1 = 0.6 \text{ V}$ $\rightarrow 6.6 \text{ V}$
 (b) $R_f = 100 \text{ k}\Omega$; $R_1 = 1 \text{ M}\Omega$; $V_1 = -1.5 \text{ V}$ $\rightarrow -1.65 \text{ V}$
 (c) $R_f = 100 \text{ k}\Omega$; $R_1 = 1 \text{ M}\Omega$; $V_1 = 5 \sin \omega t \text{ volt}$

$$1 + \frac{10^5}{10^6}$$

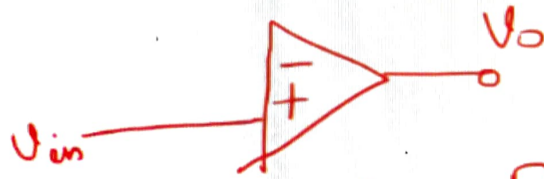

$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_{in}$$
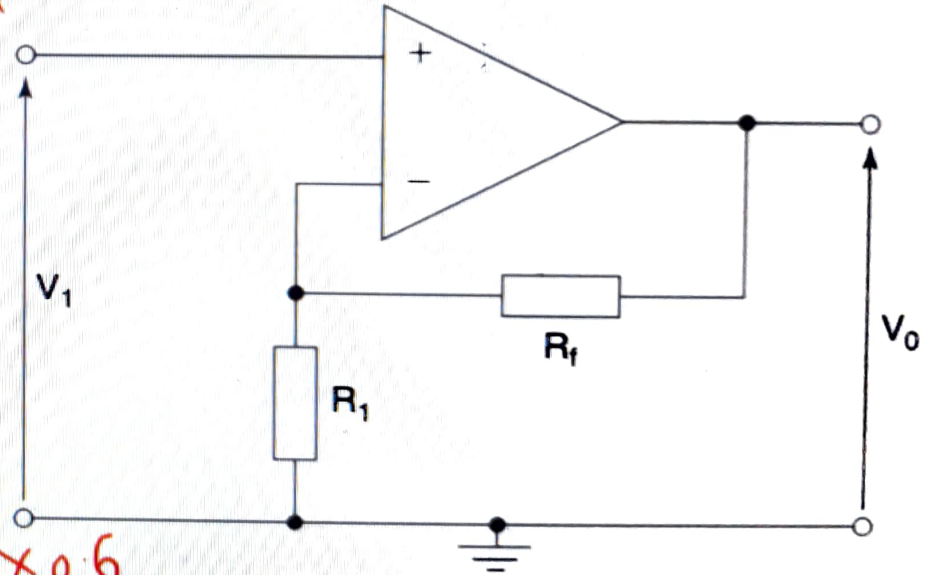
$$= \left(1 + \frac{10^6}{10^5}\right) 0.6 = 11 \times 0.6 = 6.6 \text{ V}$$



Q For the circuit of Fig. 7 the following combination of input voltages and resistors is applied. For each case calculate the resulting output voltage.

- (a) $R_1 = R_2 = 100\text{ k}\Omega$; $V_1 = 6.4\text{ V}$; $V_2 = 10.5\text{ V}$
- (b) $R_1 = R_2 = 1\text{ M}\Omega$; $V_1 = 2.6\text{ V}$; $V_2 = -4\text{ V}$
- (c) $R_1 = 100\text{ k}\Omega$; $R_2 = 1\text{ M}\Omega$; $V_1 = 4.9\text{ V}$; $V_2 = 3.8\text{ V}$

Difference op-amp

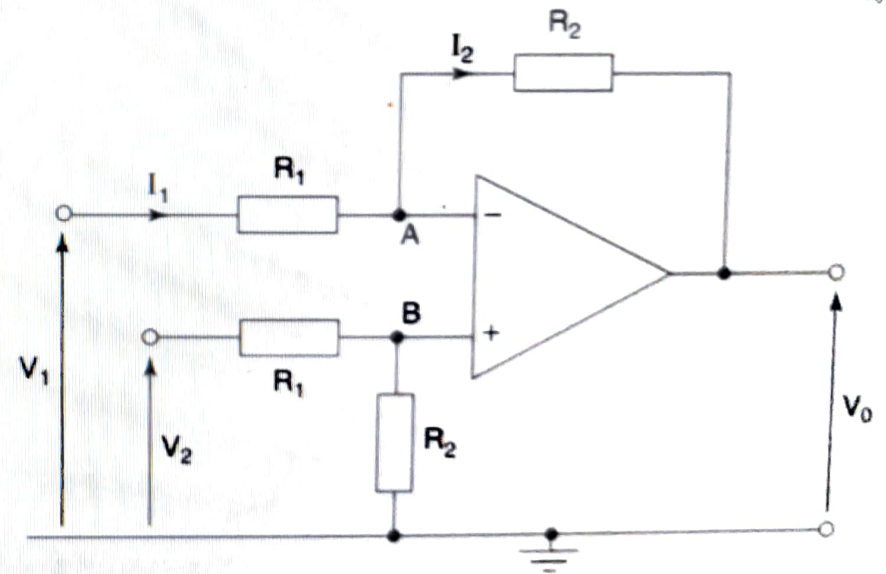


Fig. 7