
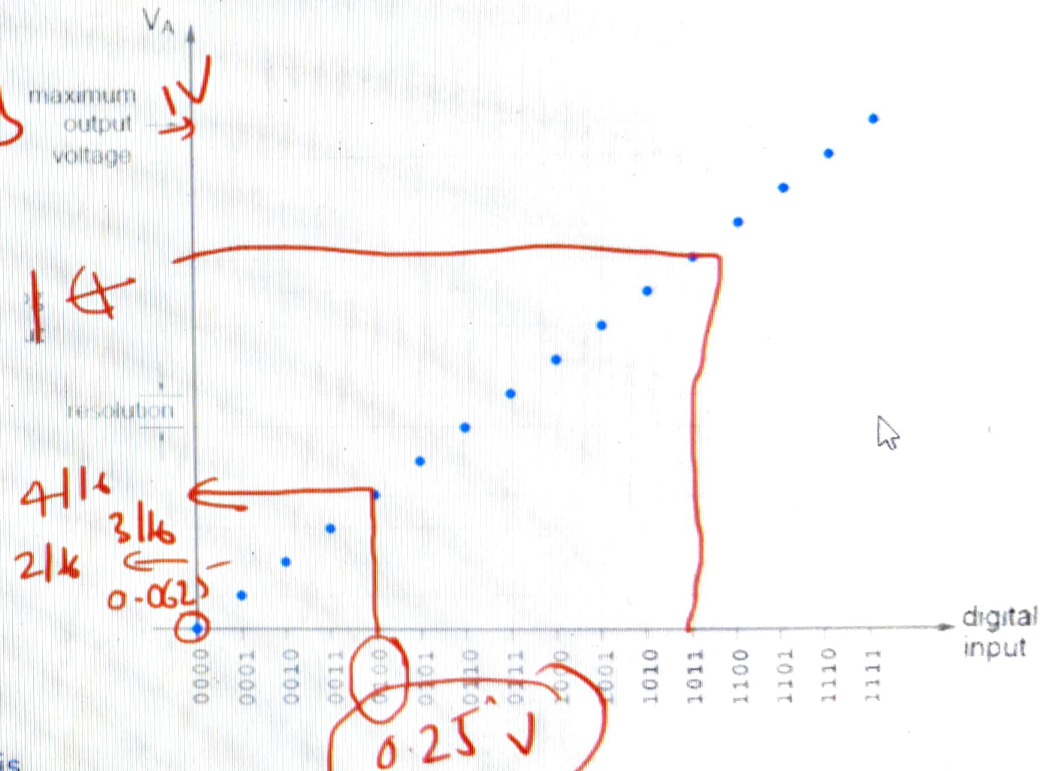


Digital to Analog Converters

max $\rightarrow 1V$
 $\frac{1}{16} =$

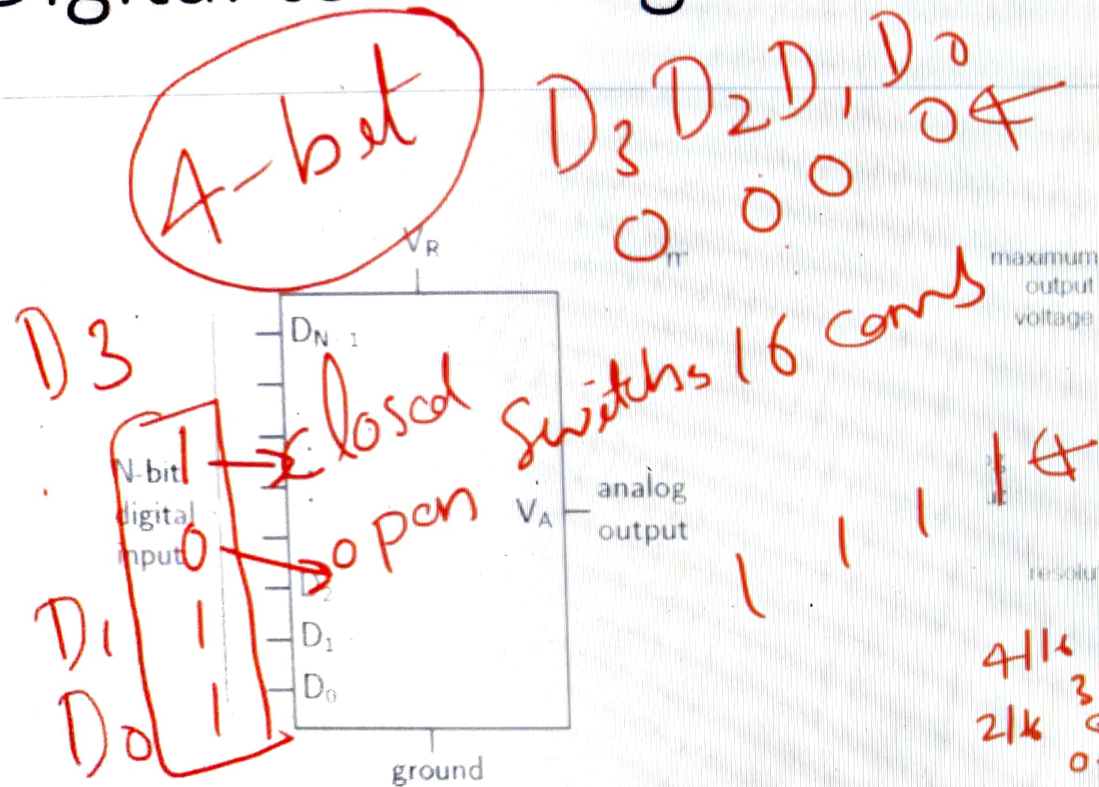


For a 4-bit DAC, with input $S_3 S_2 S_1 S_0$, the output voltage is

$$V_A = K [(S_3 \times 2^3) + (S_2 \times 2^2) + (S_1 \times 2^1) + (S_0 \times 2^0)]$$

In general, $V_A = K \sum_{k=0}^{N-1} S_k 2^k$

K is proportional to the reference voltage V_R . Its value depends on how the DAC is implemented.

DAC using Binary-weighted resistors

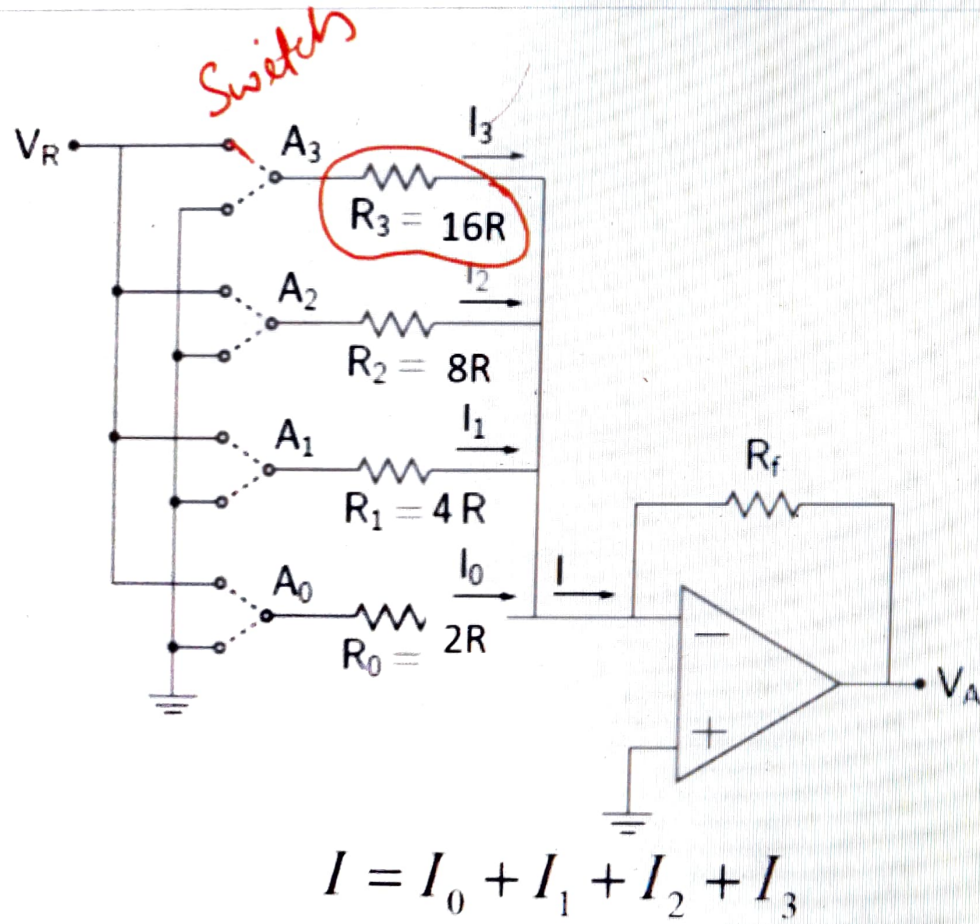


- It consists of parallel binary weighted resistor bank and a feedback resistor R_f .
- The switch positions decides the binary word (i.e. $A_0, A_1, \dots A_n$).
- In the circuit op-amp is used as current to voltage converter.

$$I_0 = \frac{A_0 V_R}{R_0}$$

$$I_1 = \frac{A_1 V_R}{R_1}$$

DAC using Binary-weighted resistors

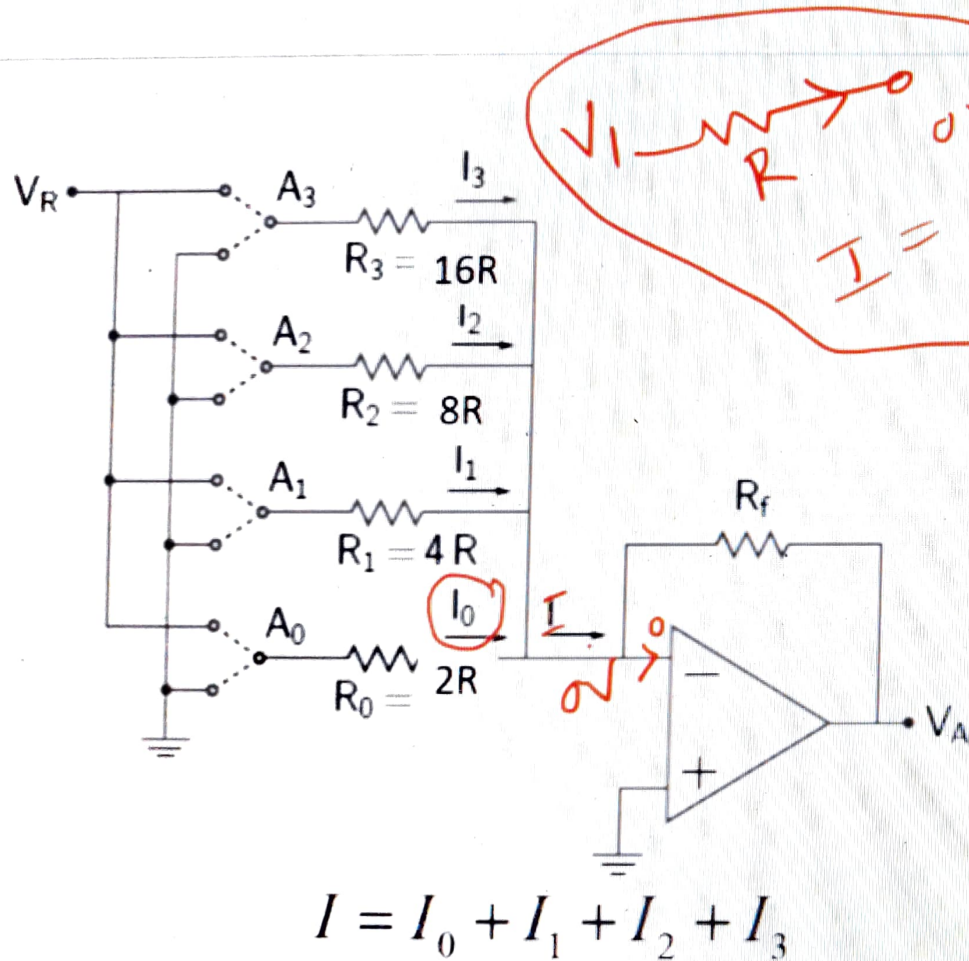


- It consists of parallel binary weighted resistor bank and a feedback resistor R_f .
- The switch positions decides the binary word (i.e. $A_0, A_1, \dots A_n$).
- In the circuit op-amp is used as current to voltage converter.

$$I_0 = \frac{A_0 V_R}{R_0} \rightarrow \frac{V_R}{R_0}$$

$$I_1 = \frac{A_1 V_R}{R_1} \quad I_2, I_3$$

DAC using Binary-weighted resistors

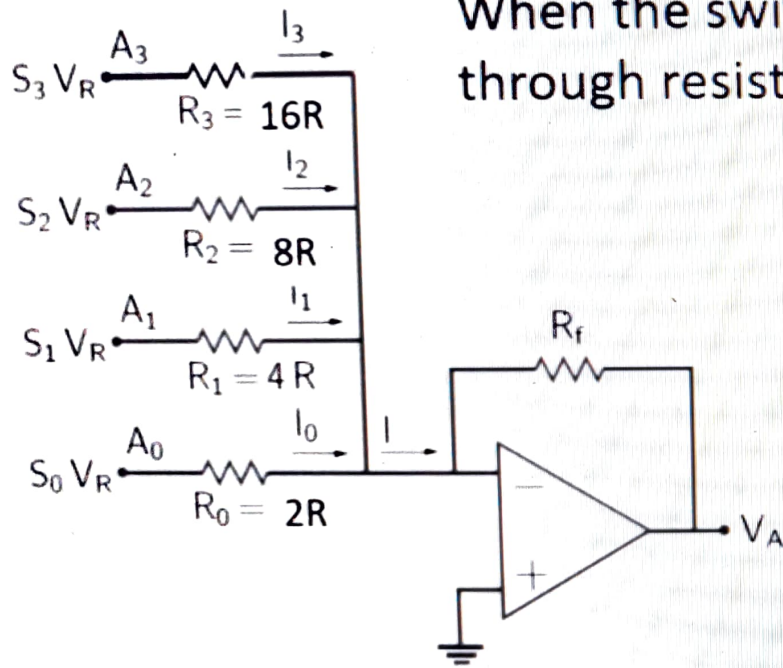

When the switches are closed the respective currents are flowing through resistors as shown in the circuit diagram

$$\therefore V_o = -IR_f$$

$$\therefore V_o = -[I_1 + I_2 + I_3 + \dots + I_n]R_f$$

$$\therefore V_o = -\left[s_0 \frac{V_R}{2^1 R} + s_1 \frac{V_R}{2^2 R} + s_2 \frac{V_R}{2^3 R} + \dots + s_n \frac{V_R}{2^n R} \right] R_f$$

$$V_o = -\frac{R_f}{R} V_R [s_0 2^{-1} + s_1 2^{-2} + s_2 2^{-3} + \dots + s_n 2^{-n}]$$

$$\text{If } R_f = R$$

$$\therefore V_o = -V_R [s_0 2^{-1} + s_1 2^{-2} + s_2 2^{-3} + \dots + s_n 2^{-n}]$$

Problems

- Consider the example of 3-bit DAC. When input binary sequence is $A_0A_1A_2 = 001$
- Consider the example of 3-bit DAC. When input binary sequence is $A_0A_1A_2 = 101$

