 


# SR latch example: Calling an air hostess

- Design a network to control a lamp from two pushbutton switches labeled S and R.
  - If we push switch S the light should turn on.
    - If we then release S, the light should stay on.
  - If we push switch R, the lamp should turn off
    - If we release R the lamp should stay off.

Assume that both S and R are not pushed at the same time.




Dr. E. Paul Brineard

9



# SR Latch with control input

 

(a) Logic diagram

$En$	$S$	$R$	Next state of $Q$
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate

(b) Function table


- In either case, when  $En$  returns to 0, the circuit remains in its current state.
- An indeterminate condition occurs when all three inputs are equal to 1

Dr. E. Paul Brineard


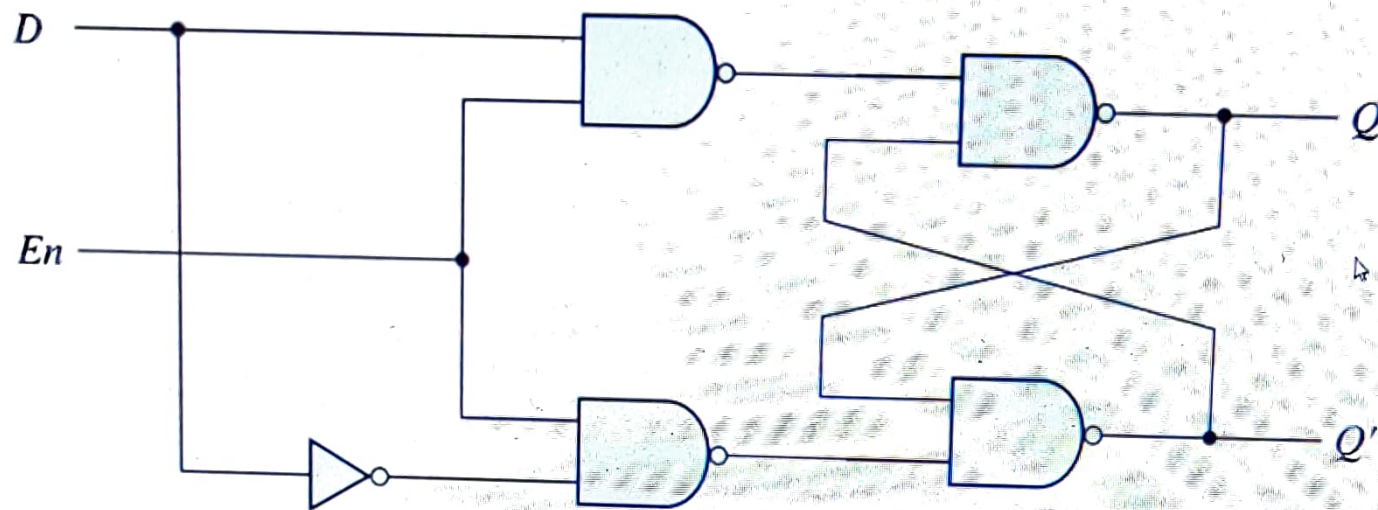
# D Latch

- One way to eliminate the undesirable condition of the indeterminate state in the SR latch is to ensure that inputs S and R are never equal to 1 at the same time. This is done in the D latch



(a) Logic diagram




$En$	$D$	Next state of $Q$
0	X	No change
1	0	$Q = 0$ ; reset state
1	1	$Q = 1$ ; set state

(b) Function table

Dr. E. Paul Brineard


   
# Graphic symbols for SR, S'R' and D latch



Dr. E. Paul Braineard



# Storage elements: Flip-flops

- The state of a flip-flop is changed by switching the control input.
- This momentary change is called a trigger
  - The transition it causes is said to “trigger the flip-flop”.
- Flip-flops are synchronous bistable devices
  - Also known as *bistable multivibrators*
  - Synchronous: the output changes state only at a specified point (leading or trailing edge) on the triggering input called the **clock** (CLK)
    - which is designated as a control input, C
    - Output changes in synchronization with the clock
    - FFs are edge-triggered
    - Latches are level triggered
- A **flip-flop**, that stores one bit
- Combine that block to build multi-bit storage – a **register**

TEJADITYA NACHIKETA P has left the meeting

Dr. E. Paul Braineard

DLD C(16Feb2021) ^



Type here to search



# Clock responses



(a) Response to positive level



(b) Positive-edge response



(c) Negative-edge response


Clock response in latch and flip-flop

# Edge-triggered flip-flop


- Changes state either at the positive edge (rising edge) or at the negative edge (falling edge) of the clock pulse
- Sensitive to the inputs only at this transition of the clock
- Two types of edge-triggered flip-flops are covered in this section
  - D FF
  - J-K FF

## Positive edge triggered

Dynamic input indicator

 

## Negative edge triggered

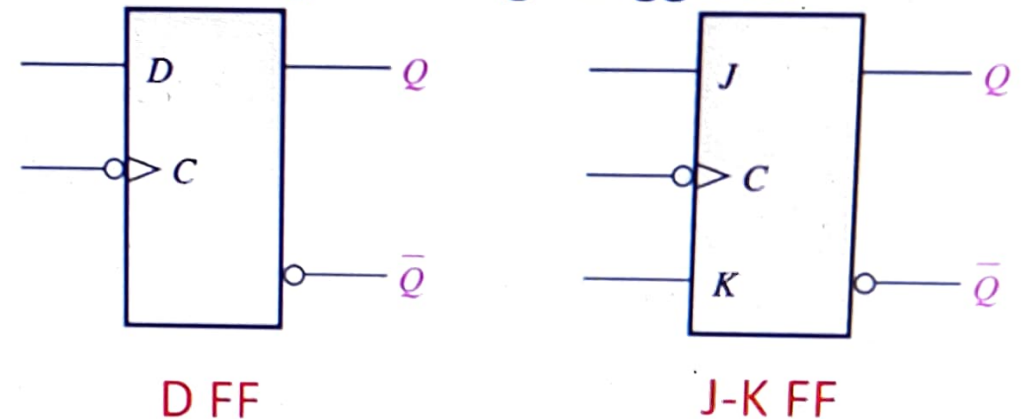


Logic symbols

Dr. E. Paul Braineard


 
# D Flip-Flop

- The  $D$  input of the **D flip-flop** is a **synchronous**
- **Data** on the input are transferred to the flip-flop's output only on the triggering edge of the clock pulse.
- When  $D$  is HIGH, the  $Q$  output goes HIGH on the triggering edge of the clock pulse, and the flip-flop is SET.
- When  $D$  is LOW, the  $Q$  output goes LOW on the triggering edge of the clock pulse, and the flip-flop is RESET



Dr. E. Paul Braineard




# Operation of a positive edge-triggered D flip-flop

- The flip-flop cannot change state except on the triggering edge of a clock pulse


Truth table for a positive edge-triggered D flip-flop.

Inputs		Outputs		Comments
D	CLK	Q	$\bar{Q}$	
0	↑	0	1	RESET
1	↑	1	0	SET

↑ = clock transition LOW to HIGH

 

 (a)  $D = 1$  flip-flop SETS on positive clock edge. (If already SET, it remains SET.)



(b)  $D = 0$  flip-flop RESETS on positive clock edge. (If already RESET, it remains RESET.)

Dr. E. Paul Brineard

# Problem

- Determine the  $Q$  and  $\bar{Q}$  output waveforms of the flip-flop in Figure 1 for the  $D$  and CLK inputs in Figure 2. Assume that the positive edge-triggered flip-flop is initially RESET.

 


Figure 1


 


Figure 2

Dr. E. Paul Braineard

# D Flip-flop

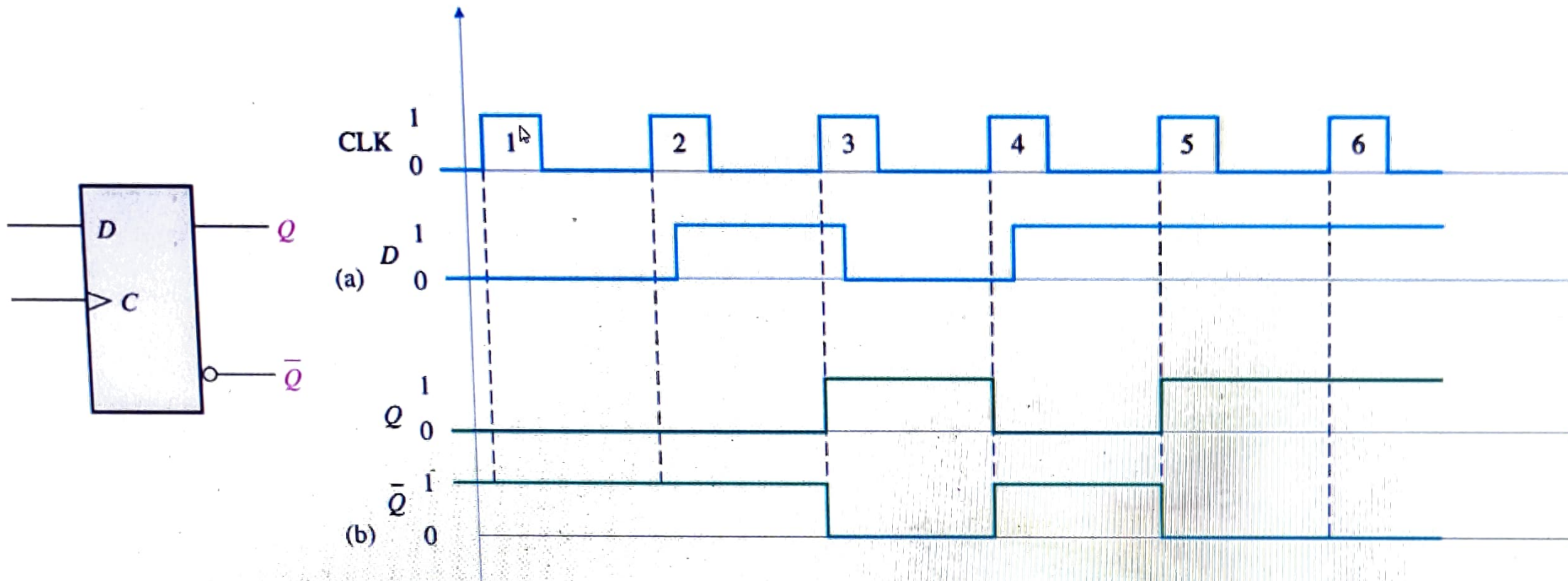





# The J-K Flip-Flop

- The  $J$  and  $K$  inputs of the **J-K flip-flop** are synchronous
  - Input data are transferred to the flip-flop's output only on the triggering edge of the clock pulse
- When  $J$  is HIGH and  $K$  is LOW, the  $Q$  output goes HIGH on the triggering edge of the clock pulse, and the flip-flop is **SET**.
- When  $J$  is LOW and  $K$  is HIGH, the  $Q$  output goes LOW on the triggering edge of the clock pulse, and the flip-flop is **RESET**.
- When both  $J$  and  $K$  are LOW, the output does not change from its prior state.
- When  $J$  and  $K$  are both HIGH, the flip-flop changes state. This called the **toggle** mode.

 
# Operation of a positive edge-triggered J-K flip-flop



 
(a)  $J = 1, K = 0$  flip-flop SETS on positive clock edge. (If already SET, it remains SET.)



 (b)  $J = 0, K = 1$  flip-flop RESETS on positive clock edge. (If already RESET, it remains RESET.)



 (c)  $J = 1, K = 1$  flip-flop changes state (toggle).



(d)  $J = 0, K = 0$  flip-flop does not change. (If SET, it remains SET; if RESET, it remains RESET.)