

Gate-Level Minimization

Karnaugh map or K-map

Gate-Level Minimization

- Design task of finding an optimal gate-level implementation of the Boolean functions describing a digital circuit
- The complexity of implementing digital logic gates is directly related to the complexity of the algebraic expression
- Simple straightforward procedure for minimizing Boolean functions is
 - Karnaugh map or K-map

Karnaugh map

- Diagram of squares
- Each square represents one minterm of the function that is to be minimized

Two-variable K-map

- Two variables
- Four minterms
- The K-map consists of four squares, one for each minterm

m_0	m_1
m_2	m_3

		y	
		0	1
x	0	$x'y'$	$x'y$
	1	xy'	xy

00	01
10	11


0	0
0	1
1	0
1	1

Two-variable K-map

- Minimize the function $m_1 + m_2 + m_3$
- $m_1 + m_2 + m_3 = x'y + xy' + xy = x + y$

m_0	m_1
m_2	m_3

$x'y'$	$x'y$
xy'	xy

 

$x + y$

Three-variable K-map

- Three variable K-map
- There are eight minterms
- \therefore Eight squares
- Characteristic: **Only one bit changes**

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

		y			
		yz			
		00	01	11	10
x	0	$x'y'z'$	$x'y'z'$	$x'y'z'$	$x'y'z'$
	1	$x'y'z'$	$x'y'z'$	$x'y'z'$	$x'y'z'$

Three-variable K-map

- Simplify the Boolean function $F(x, y, z) = \Sigma(2, 3, 4, 5)$
- $xy' + x'y$

		y			
		yz			
		00	01	11	10
x	0	0	0	1	1
x	1	1	1	0	0
		z			