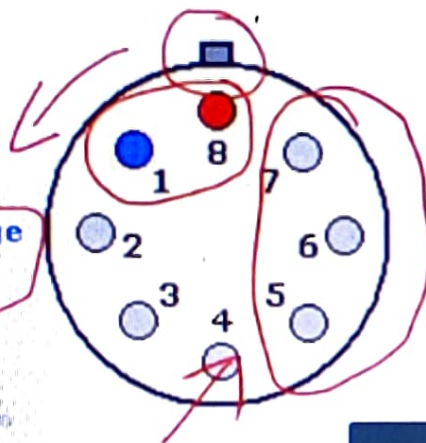


555 Timer


- First introduced around 1971 by the Signetics Corporation as the SE555/NE555 and was called “The IC Time Machine”
- Highly stable device for generating accurate
 - Time delay ✓
 - Oscillations ✓
- Supply range: +5V to +18 V

1. Ground
2. Trigger
3. Output
4. Reset
5. Control Voltage
6. Threshold
7. Discharge
8. Vcc (+)



(c) Tony van Roon

fig. 1. 8-pin T pack

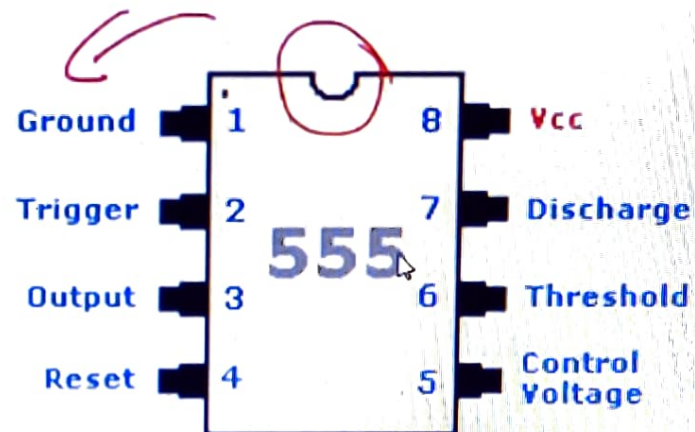

Are you talking? Your mic is off.
Click the mic to turn it on.

Functional diagram of 555 Timer

- Resistive divider
n/w
- Two comparators
- Two transistors
- One SR FF
- Inverter

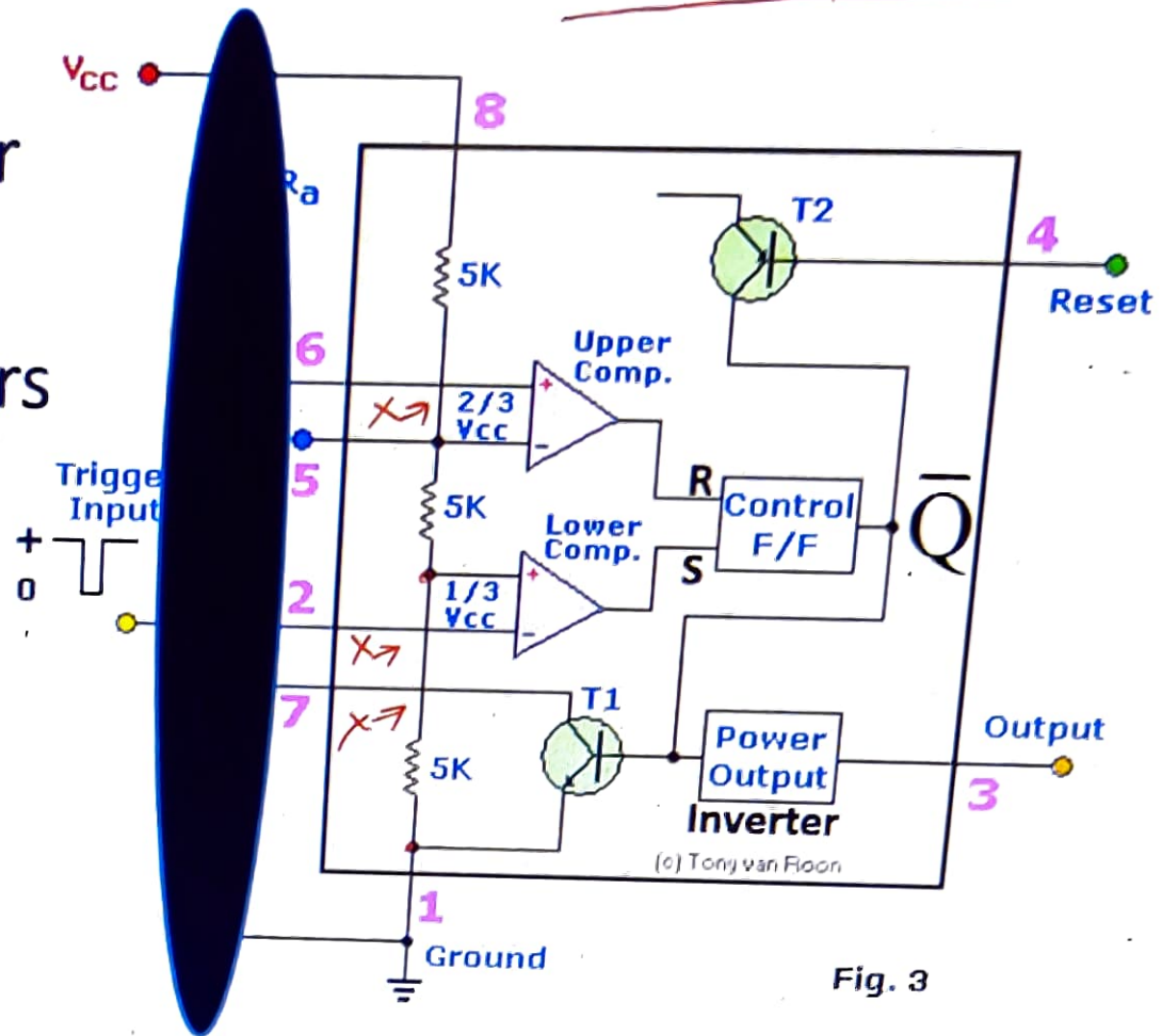


Fig. 3

Operation of 555 Timer

- In the standby/stable state
 - The output of FF \bar{Q} is high
 - Output is low
- Negative going trigger pulse is applied to pin 2
 - As it goes less than $V_{CC}/3$, output of LC goes high, Q = high and \bar{Q} is low
- Threshold voltage at pin 6 as it passes $(2/3)V_{CC}$, the output of UC goes high, and resets FF. Q = low and \bar{Q} is high

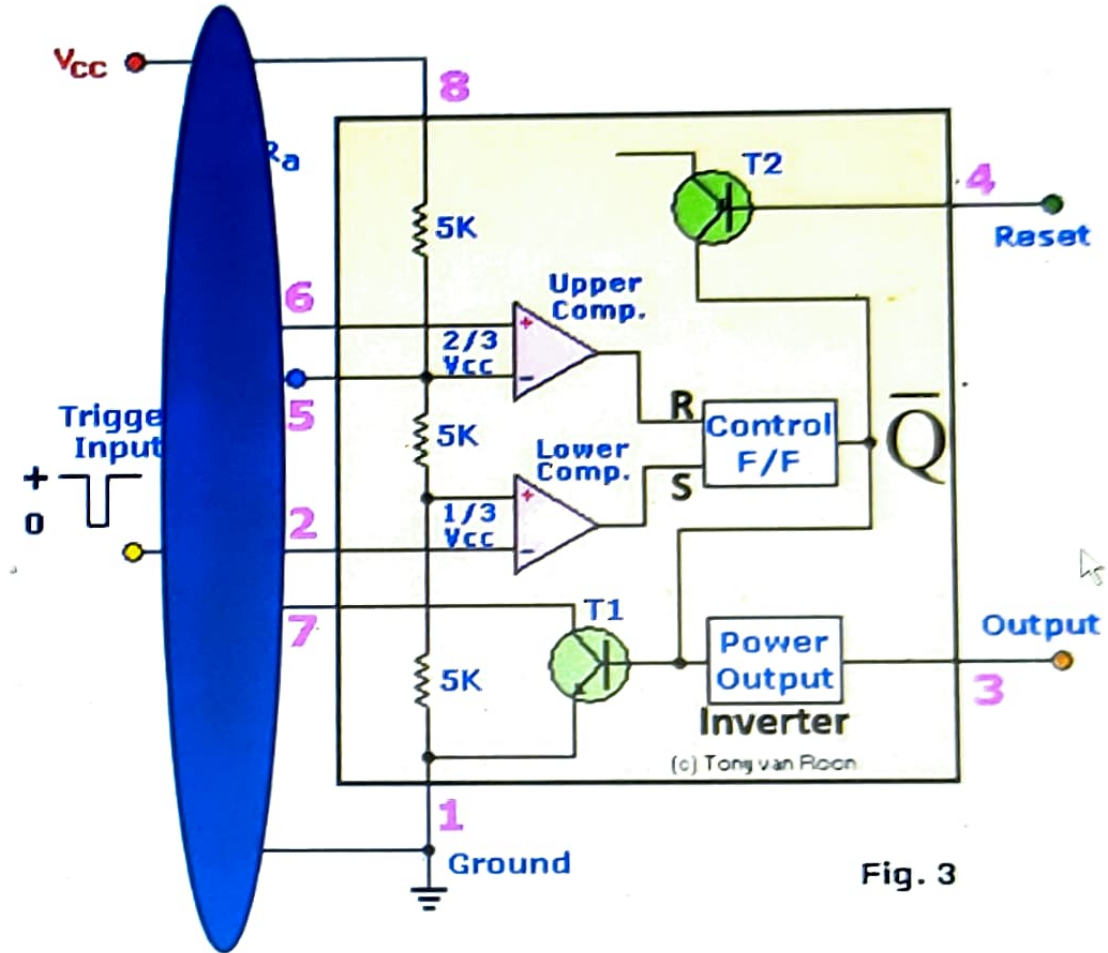


Fig. 3

Operation modes of 555 timer

- Monostable mode
 - circuit generates a single pulse of a fixed time duration each time it receives an input trigger pulse
 - Duration is controlled by RC network
- Astable mode
 - simply an oscillator
 - generates a continuous stream of rectangular on-off pulses
 - The frequency of the pulses and their duty cycle are dependent upon the RC network values.