

First order low pass active filter

The voltage V_1 across the capacitor C in the s -domain is

$$V_1(s) = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} V_i(s)$$

So,

$$\frac{V_1(s)}{V_i(s)} = \frac{1}{RCs + 1}$$

where $V(s)$ is the Laplace transform of v in time domain.


The closed loop gain A_o of the op-amp is,

$$A_o = \frac{V_o(s)}{V_1(s)} = \left(1 + \frac{R_f}{R_i} \right)$$

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{V_o(s)}{V_1(s)} \cdot \frac{V_1(s)}{V_i(s)} = \frac{A_o}{RCs + 1}$$

Let $\omega_h = \frac{1}{RC}$

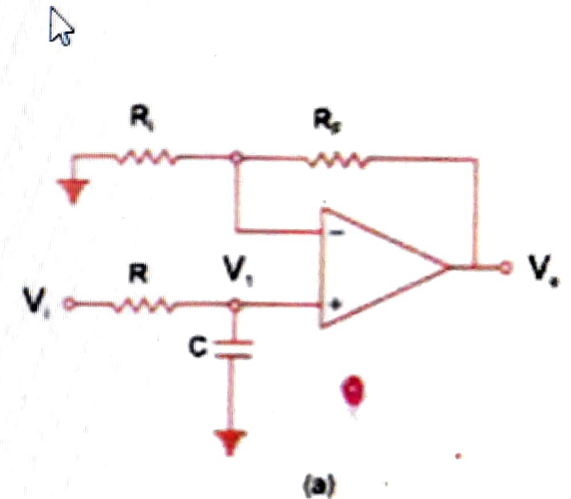Therefore,
$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{A_o}{\frac{s}{\omega_h} + 1} = \frac{A_o \omega_h}{s + \omega_h}$$



$K = \frac{V_o}{V_i}$ (gain)
 gain in dB
 $\rightarrow \log_{10}\left(\frac{V_o}{V_i}\right) \rightarrow \text{dB}$

First order low pass active filter

The voltage V_1 across the capacitor C in the s -domain is

$$V_1(s) = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} V_i(s)$$

So,
$$\frac{V_1(s)}{V_i(s)} = \frac{1}{RCs + 1}$$

where $V(s)$ is the Laplace transform of v in time domain.

The closed loop gain A_o of the op-amp is,


$$A_o = \frac{V_o(s)}{V_1(s)} = \left(1 + \frac{R_F}{R_i}\right)$$

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{V_o(s)}{V_1(s)} \cdot \frac{V_1(s)}{V_i(s)} = \frac{A_o}{RCs + 1}$$


Let $\omega_h = \frac{1}{RC}$


Therefore,
$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{A_o}{\frac{s}{\omega_h} + 1} = \frac{A_o \omega_h}{s + \omega_h}$$

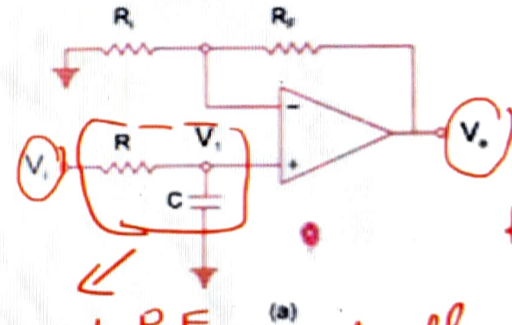impedance ① frequency $(j\omega)$
 ② s -domains $(s = j\omega)$



L P F
 cut off corner

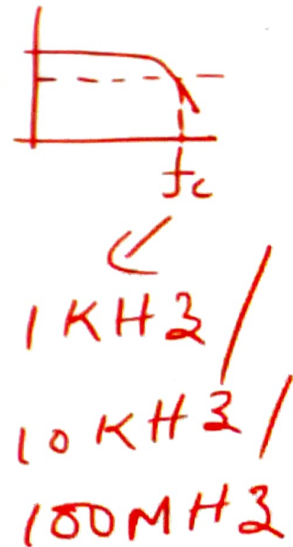

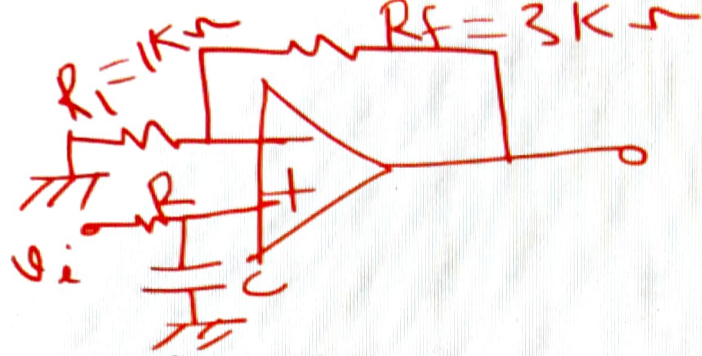

$C = 1 \mu F$ X large size
 let $C = 47 \mu F$
 R

Design an active lowpass filter with a gain of 4,
 a corner frequency of 1 kHz

$$1 + \frac{R_f}{R_1} = 4 \Rightarrow \frac{R_f}{R_1} = 3$$

$$\omega_n = \frac{1}{RC}$$

let $R_1 = 1 k\Omega$


$R_f = 3 k\Omega$

$$f_n = \frac{1}{2\pi RC}$$

let $C = 1 \mu F \Rightarrow 10^3 = \frac{1}{2\pi R(10^{-6})} \Rightarrow R = 0.159 k\Omega$
 $= 159 \Omega$

Design an active highpass filter with a gain of 10, a corner frequency of 20 kHz


$$1 + \frac{R_f}{R_1} = 10$$

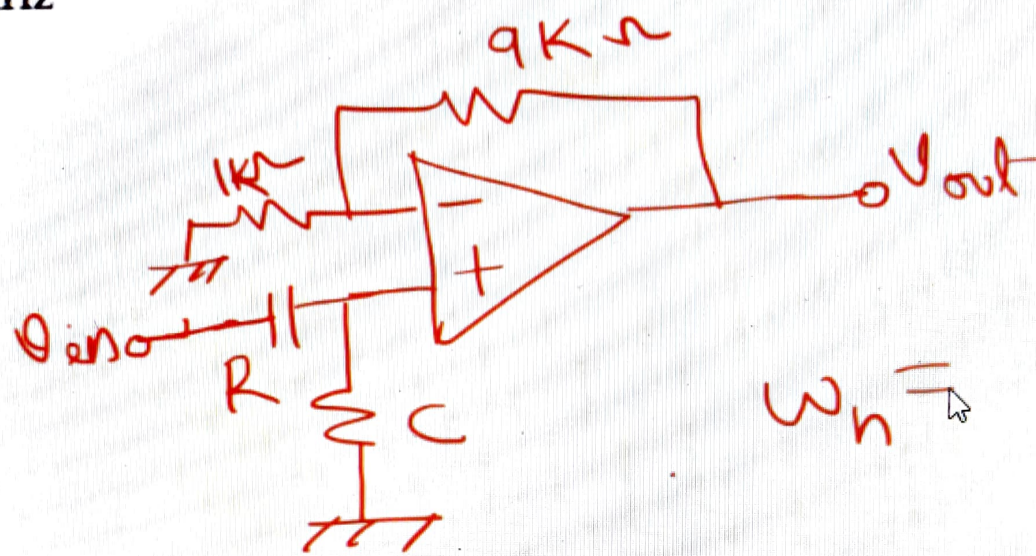

$$\omega_n =$$

Filter classification

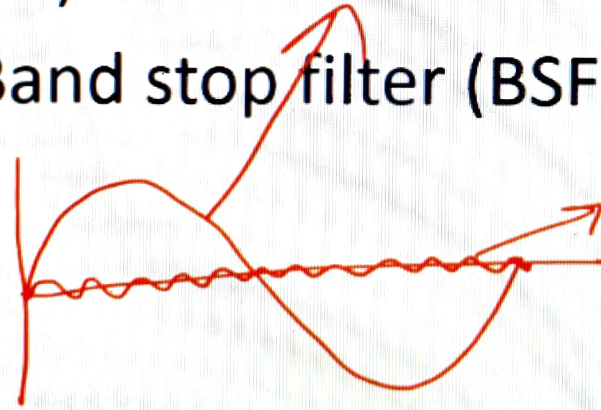- Low pass filter (LPF)
- High pass filter (HPF)
- Band pass filter (BPF)
- Band reject filter/Band stop filter (BSF)



noise
we want to remove noise
HF & low magnitude