
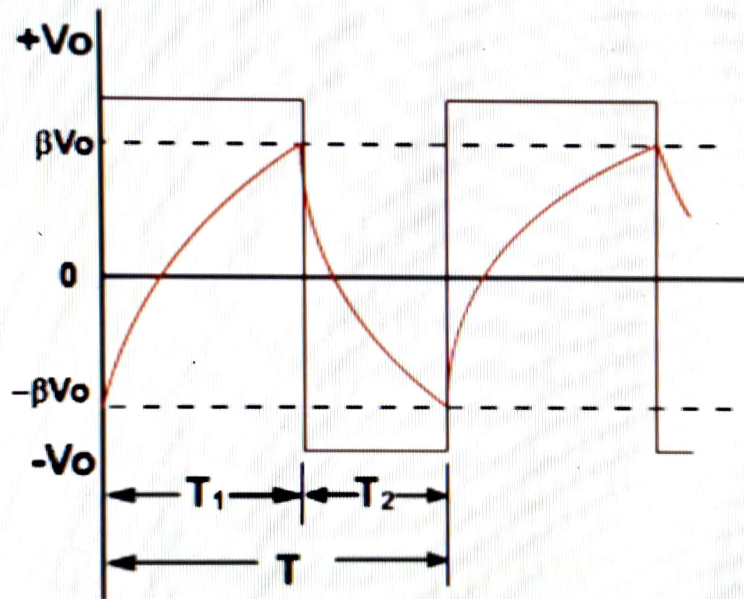


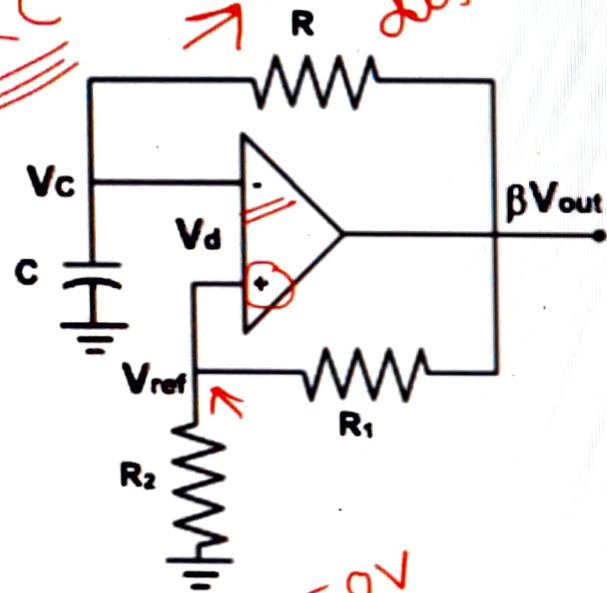Square wave generator (Astable multivibrator)



$$\beta = \frac{R_2}{R_1 + R_2}$$

$$V_{ref} = \frac{R_2}{R_1 + R_2} V_{sat}$$

$$= \beta V_{sat}$$

energy storage element
RC
store
discharge

$V_{ref} = 0V$

Square wave generator (Astable multivibrator)

- Let, $v_o = +V_{sat}$

Voltage across the capacitor

$$v_c(t) = V_f + (V_i - V_f)e^{-t/RC}$$

Final value, $V_f = +V_{sat}$

Initial value, $V_i = -\beta V_{sat}$

$$\therefore v_c(t) = V_{sat} - V_{sat}(1 + \beta)e^{-t/RC}$$



At $t = T_1$

$$v_c(T_1) = \beta V_{sat}$$

$$\beta V_{sat} = V_{sat} - V_{sat}(1 + \beta)e^{-T_1/RC}$$

Solving
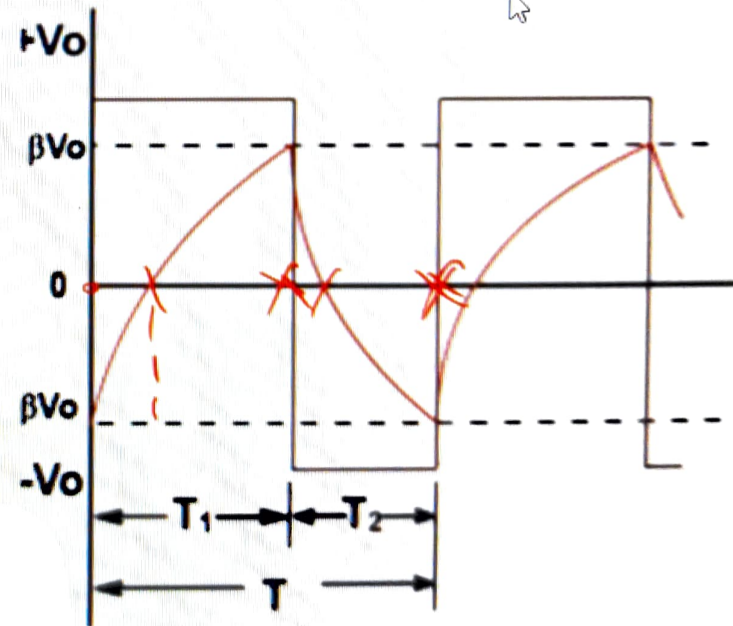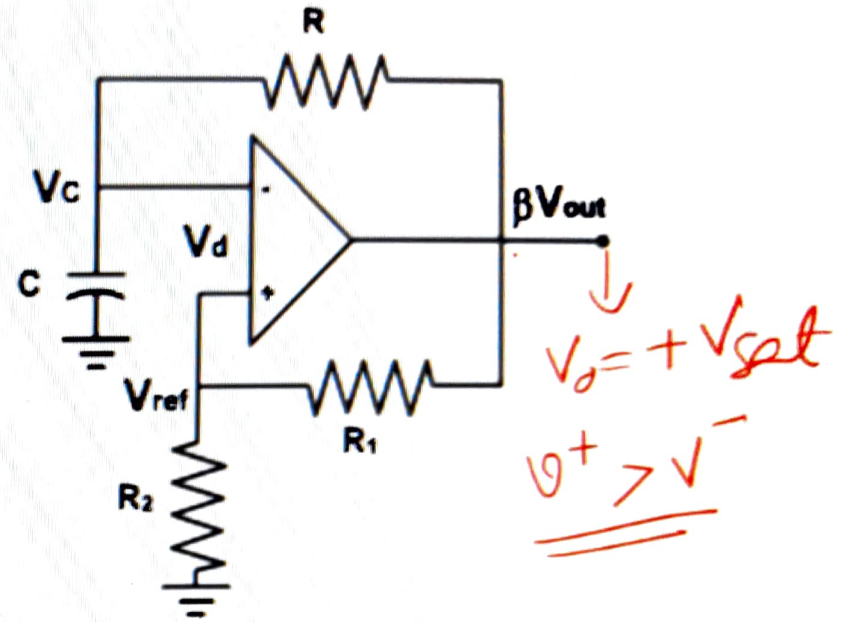
$$T_1 = RC \ln \left(\frac{1 + \beta}{1 - \beta} \right)$$



Design of square wave generator

Let the frequency of oscillation be 1 kHz

Take $\beta = 0.5$ and $R_1 = R_2 = 10 \text{ k}\Omega$.


Frequency, $f = \frac{1}{2RC \ln 3}$ Assume $C = 0.1 \text{ }\mu\text{F}$

$$\text{Then, } R = \frac{1}{2Cf \ln 3} = \frac{1}{2 \times 0.1 \times 10^{-6} \times 1000 \times \ln 3} = 4.55 \text{ k}\Omega$$



Select standard value of $4.7 \text{ k}\Omega$ for R .

Square wave generator (Astable multivibrator)

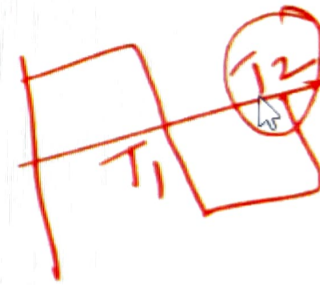- If $R_1 = R_2 = R$
 - Expression for period = $T_1 = 2RC \ln\left(\frac{2+R}{2-R}\right)$
 - The frequency of oscillation =



Square wave generator

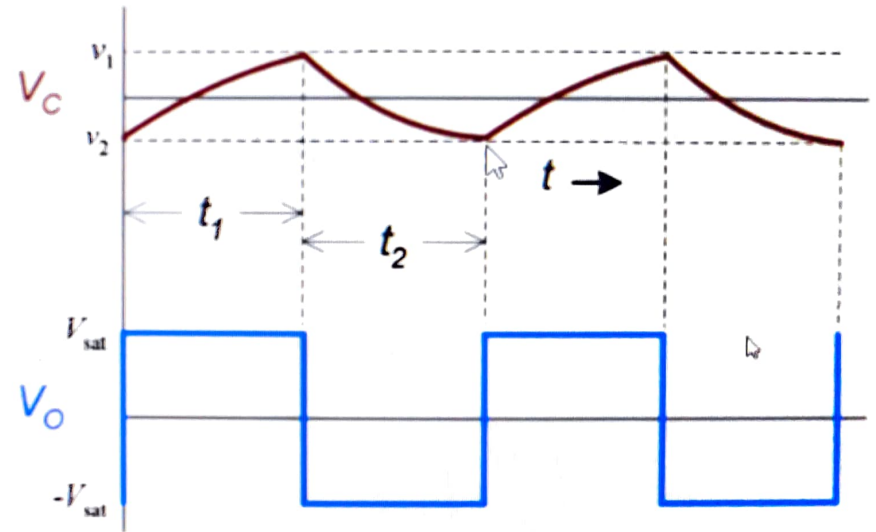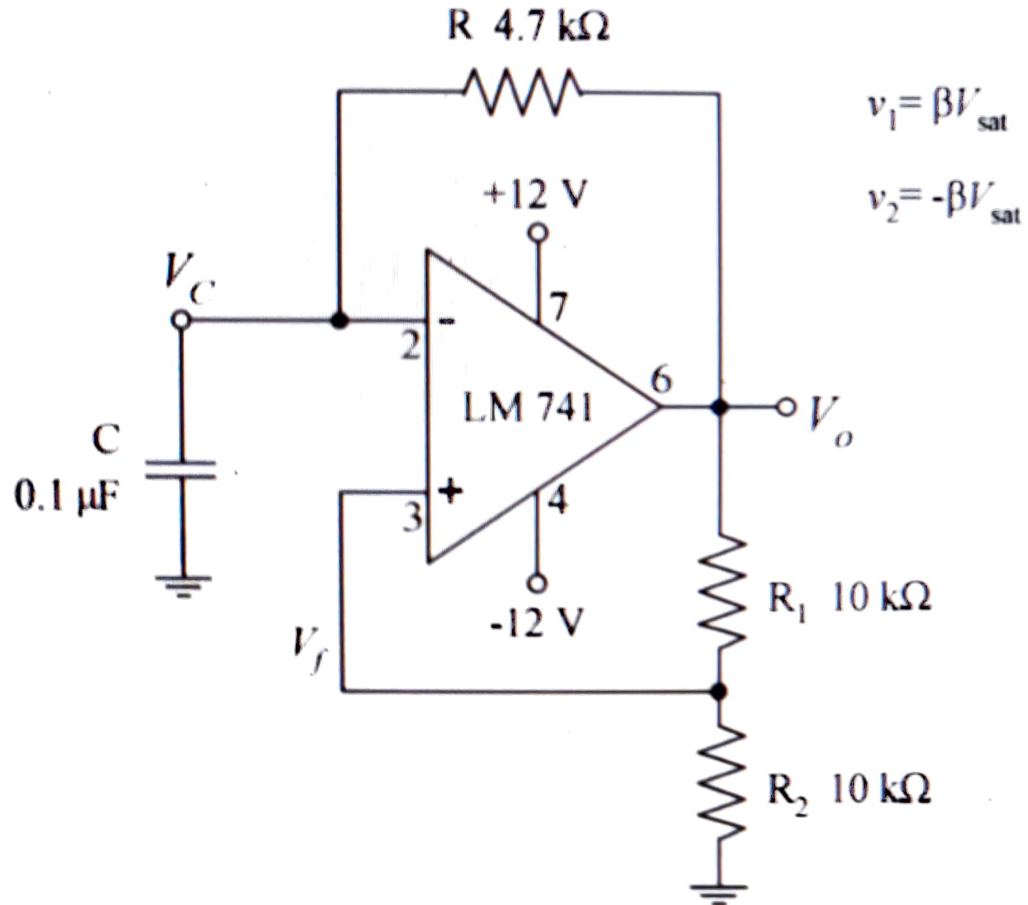

Triangular waveform generator

