

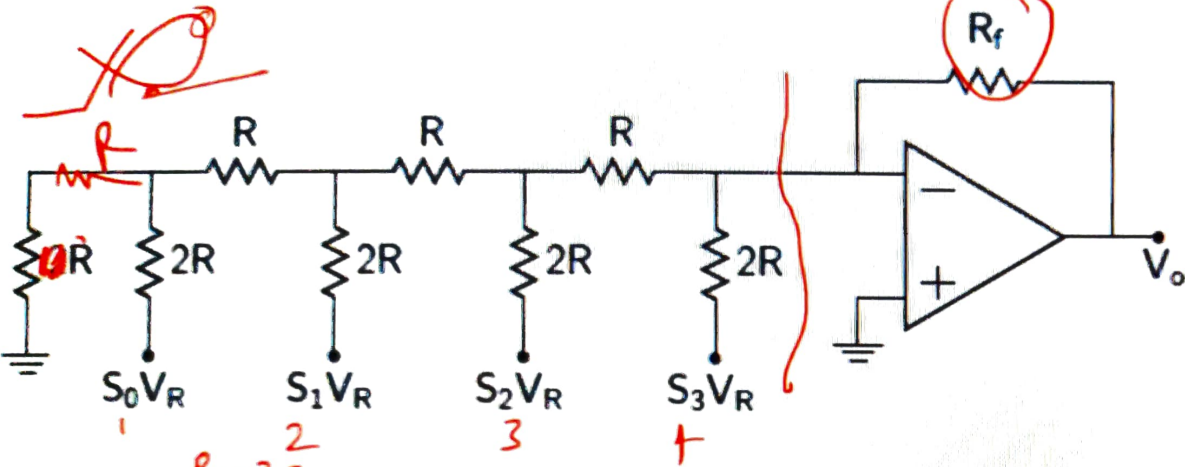
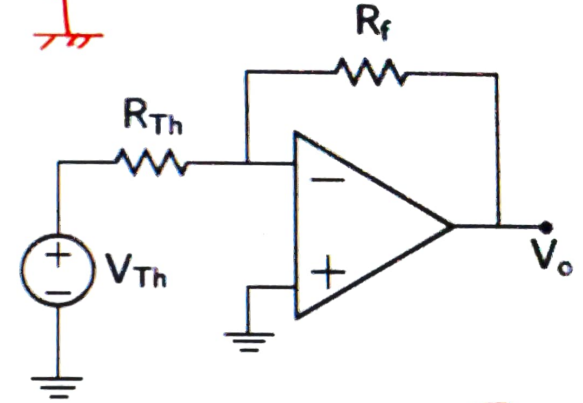


# DAC with R-2R Ladder

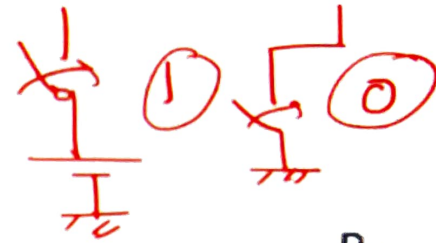

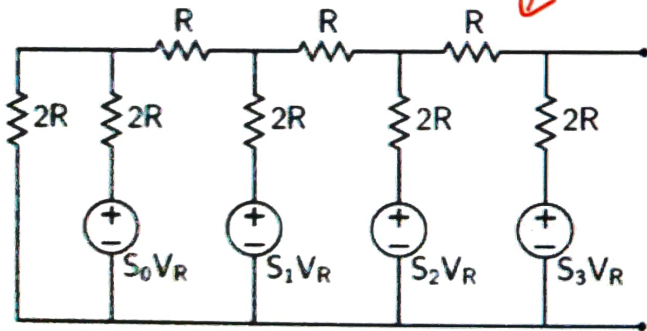The ~~original~~ network is equivalent to





Thevenin's  $\rightarrow R$   
 $\rightarrow V$

$S \rightarrow$  represents  
 status of switch

$\rightarrow 0$  (or)  $1$



# DAC with R-2R Ladder

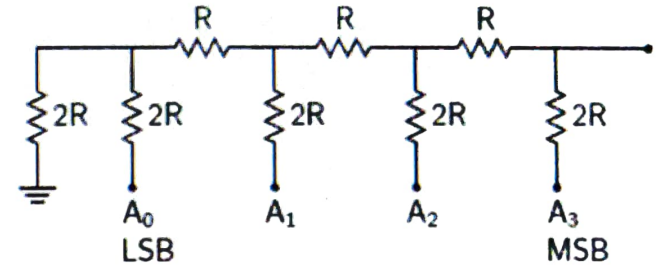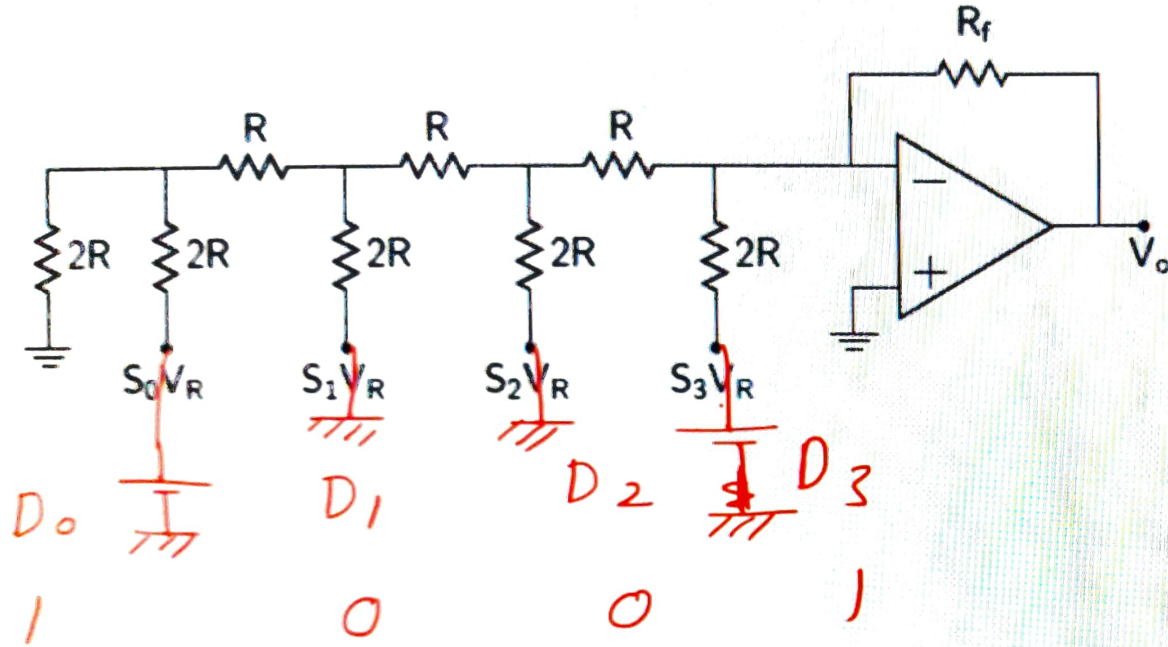


Node  $A_k$  is connected to  $V_R$  if input bit  $S_k$  is 1; else, it is connected to ground.



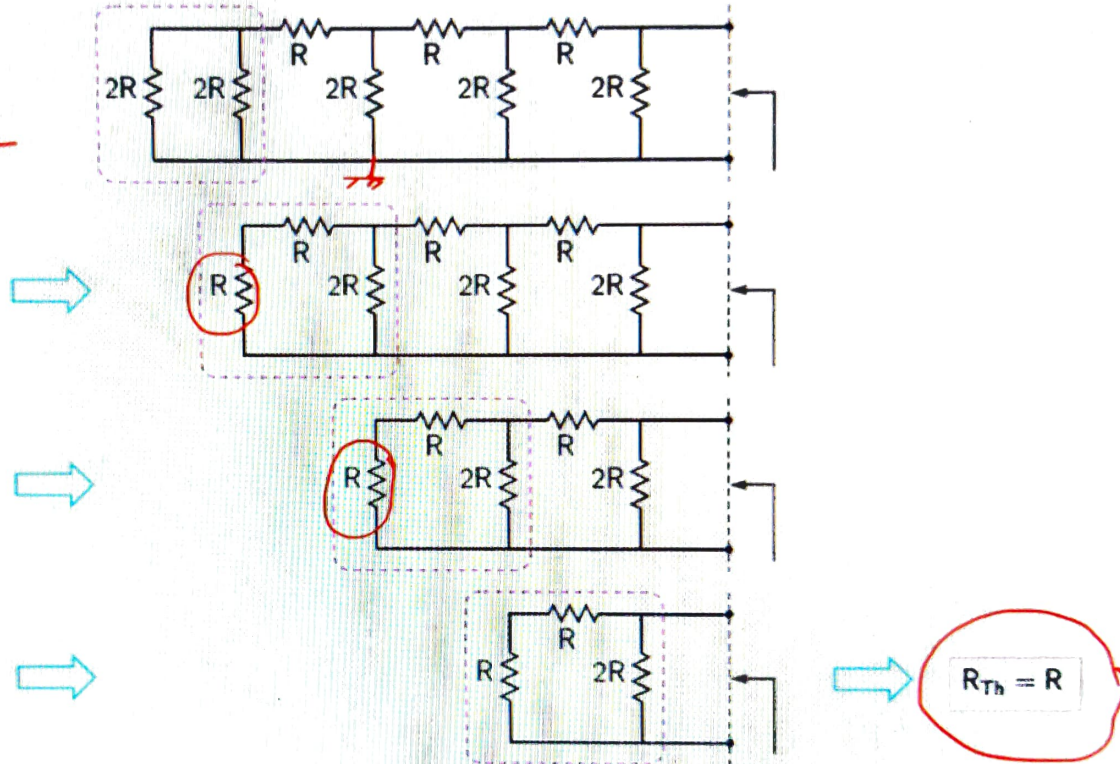
# R-2R Ladder Network: Equivalent resistance

If all the inputs are grounded.

Req =  $\frac{R}{2} \times \frac{2R}{2} = R$


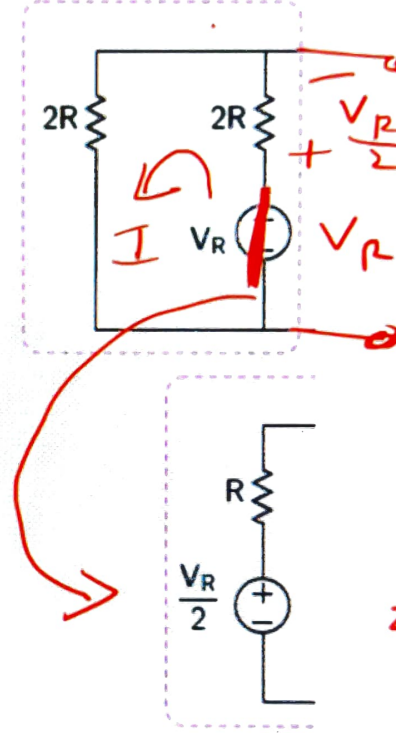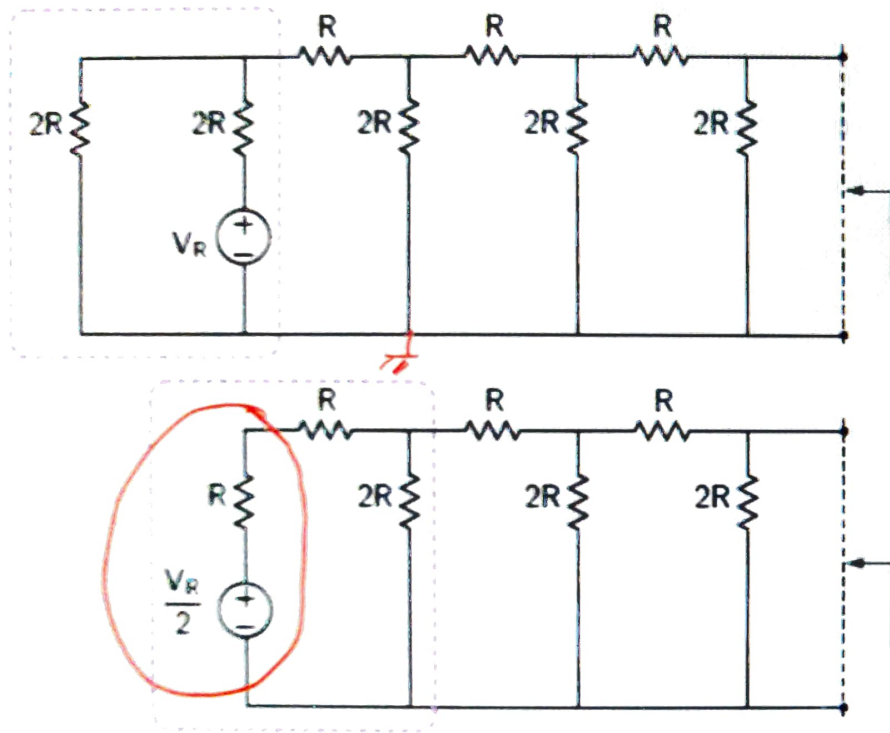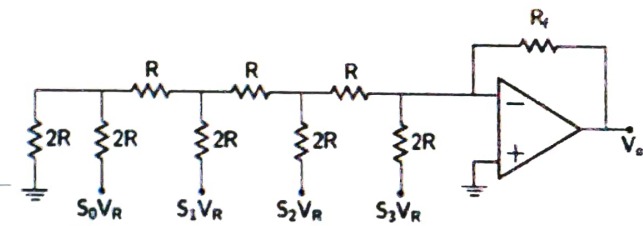
# R-2R ladder network: $V_{Th}$ for $S_0 = 1$



Handwritten notes and calculations:

LSB





$I = \frac{V_R}{4R}$

$V_{2R} = \frac{V_R}{4R} \cdot 2R = \frac{V_R}{2}$








Diagram of two 2R resistors in parallel.



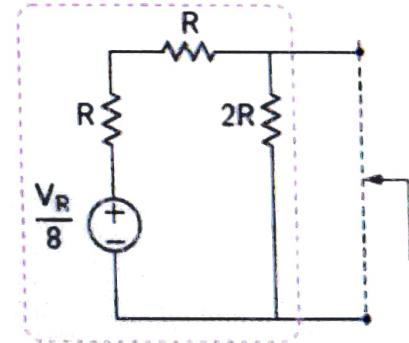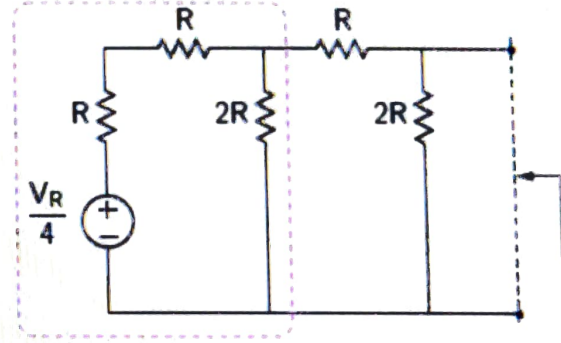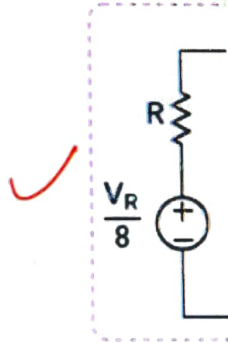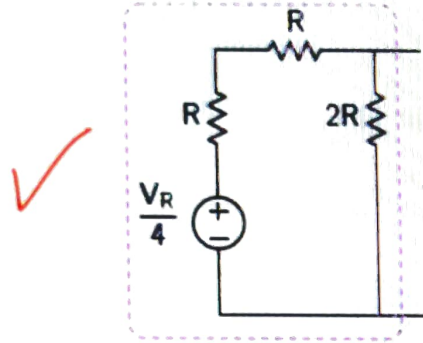
# R-2R ladder network: $V_{Th}$ for $S_0 = 1$



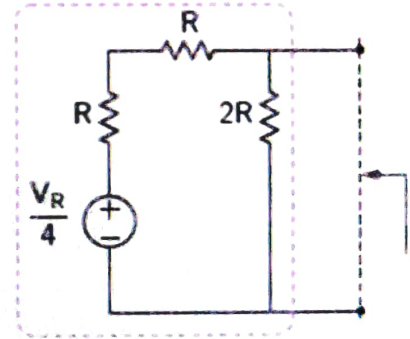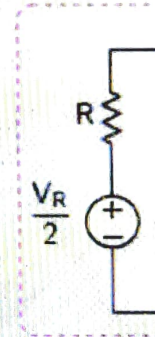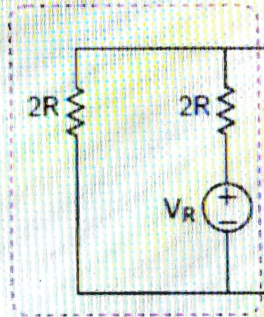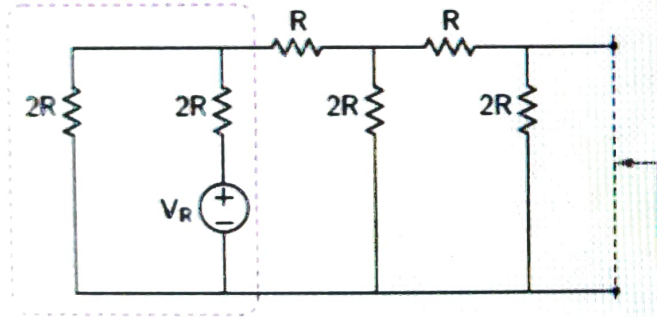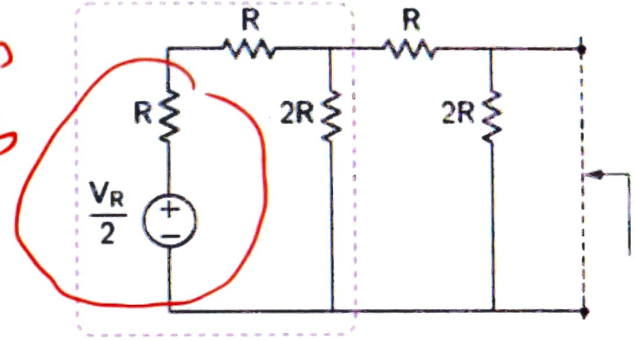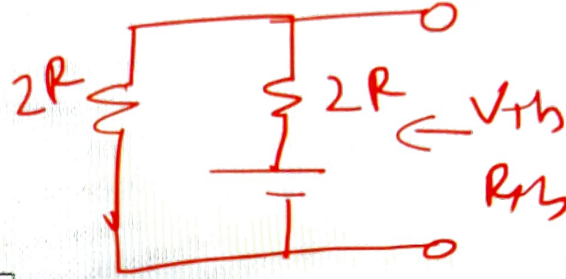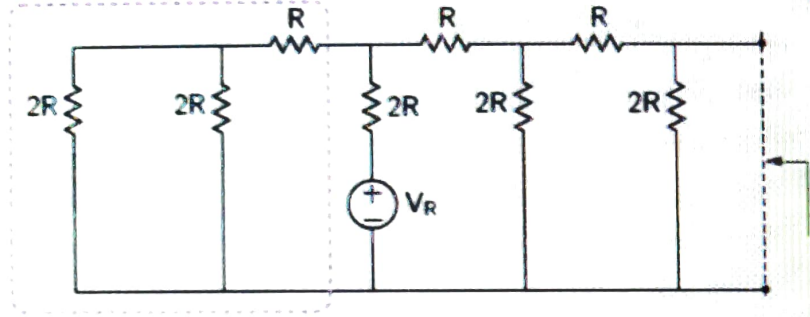R-2R ladder network:  $V_{Th}$  for  $S_1 = 1$



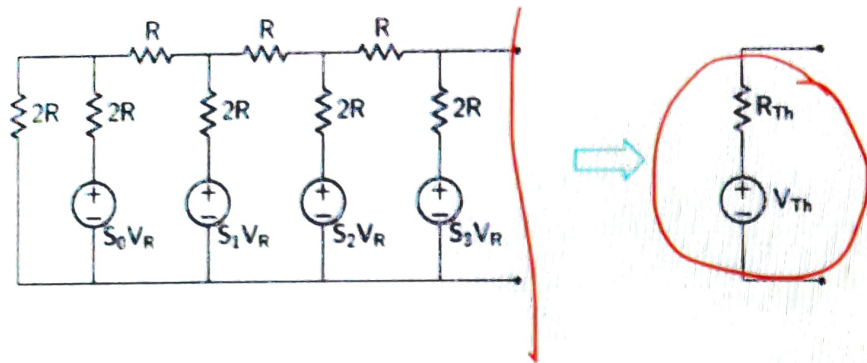


$$R_{Th} = R$$

$$V_{Th} = V_{Th}^{(S_0)} + V_{Th}^{(S_1)} + V_{Th}^{(S_2)} + V_{Th}^{(S_3)}$$

$$= \frac{V_R}{16} [S_0 2^0 + S_1 2^1 + S_2 2^2 + S_3 2^3]$$

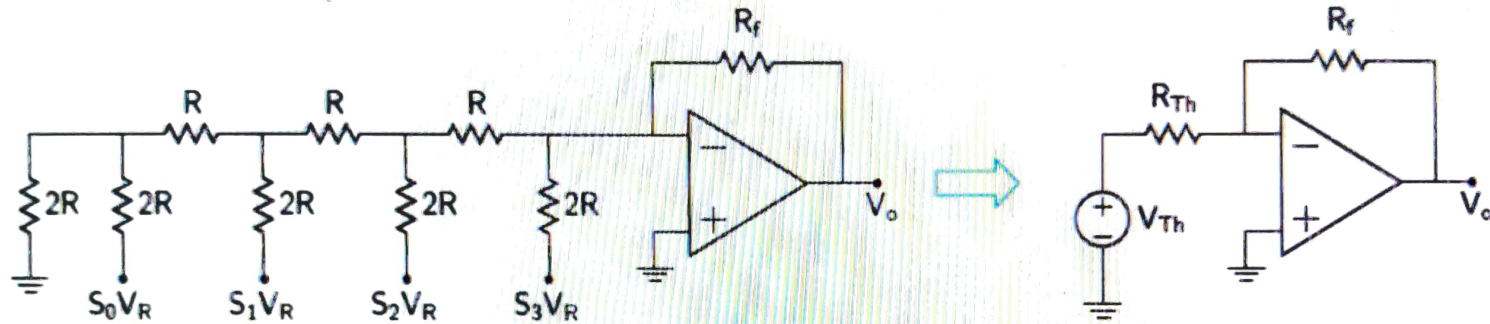We can use the  $R$ - $2R$  ladder network and an Op Amp



$$V_o = -\frac{R_f}{R_{Th}} V_{Th} = -\frac{R_f}{R_{Th}} \frac{V_R}{16} [S_0 2^0 + S_1 2^1 + S_2 2^2 + S_3 2^3]$$

$$\text{For an } N\text{-bit DAC, } V_o = -\frac{R_f}{R_{Th}} V_{Th} = -\frac{R_f}{R_{Th}} \frac{V_R}{2^N} \sum_{k=0}^{N-1} S_k 2^k.$$

6- to 20-bit DACs based on the  $R$ - $2R$  ladder network are commercially available in monolithic form (single chip)


# R-2R Ladder

- Design a 3 bit R-2R ladder DAC, and determine  $V_o$  for the following input sequences, (a) 010 (b) 011 (c) 100, and (d) 101.

$$\text{For an N-bit DAC, } V_o = -\frac{R_f}{R_{Th}} V_{Th} = -\frac{R_f}{R_{Th}} \frac{V_R}{2^N} \sum_{k=0}^{N-1} S_k 2^k.$$



# Integrated Circuits

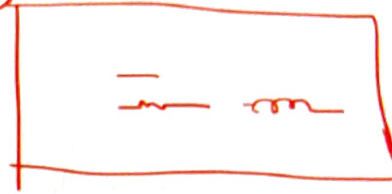


□ silicon

- How are they made
  - Diodes
  - BJTs
  - MOSFETs
- Material
  - Silicon
- Size
  - Micrometer ( $10^{-6}$  m), nm ( $10^{-9}$  m)
- Where they are made
  - Microfabrication unit (Specialized units)

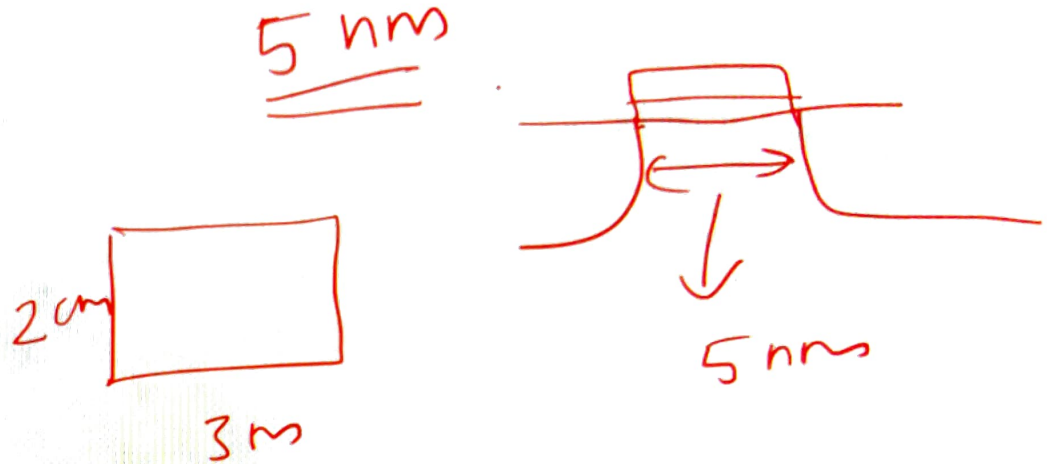
# Integrated Circuits

- How are they made
  - Diodes
  - BJTs
  - MOSFETs
- Material
  - Silicon
- Size
  - Micrometer ( $10^{-6}$  m), nm ( $10^{-9}$  m)
- Where they are made
  - Microfabrication unit (Specialized units)



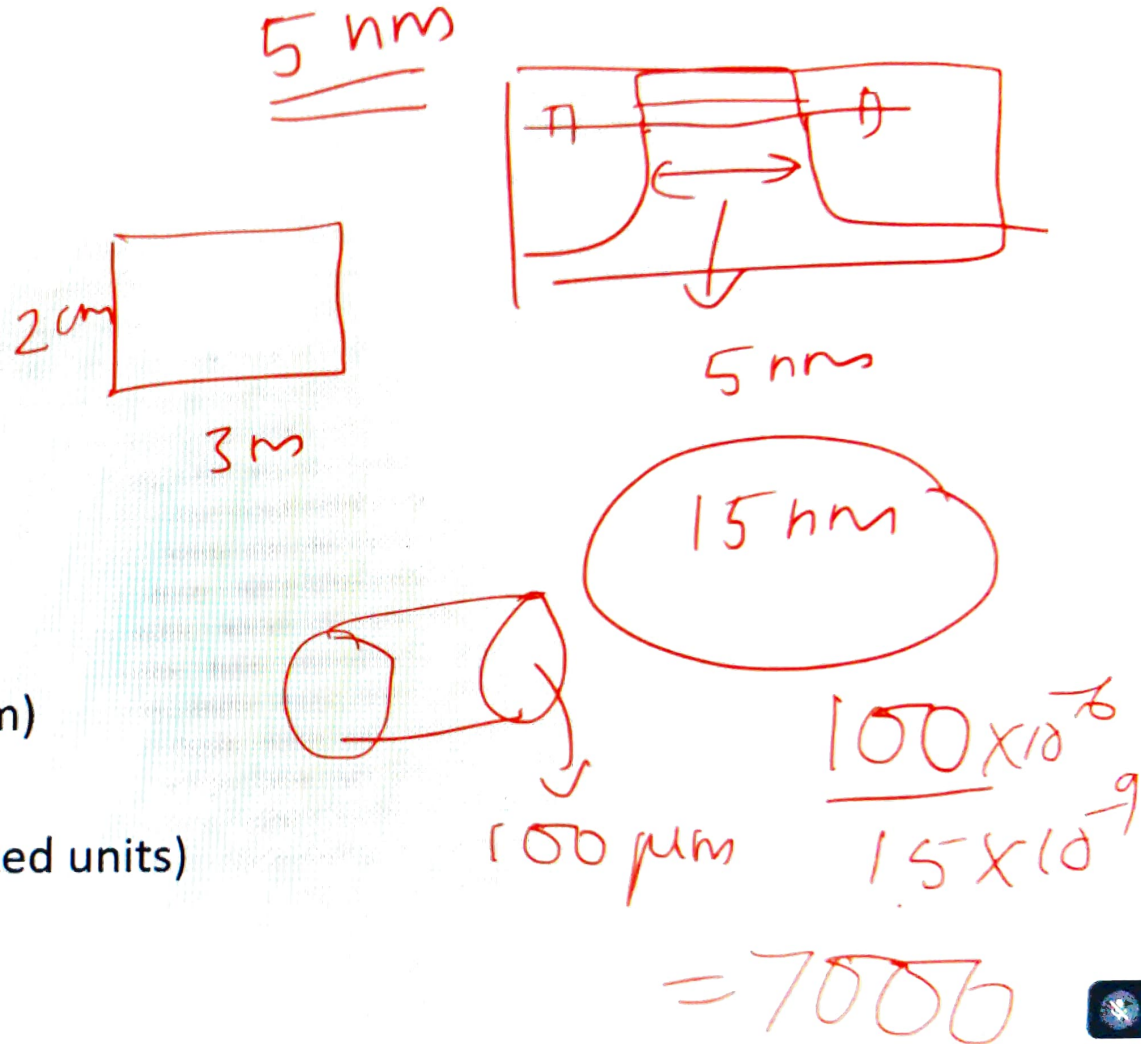
# Integrated Circuits



- How are they made
  - Diodes
  - BJTs
  - MOSFETs
- Material
  - Silicon
- Size
  - Micrometer ( $10^{-6}$  m), nm ( $10^{-9}$  m)
- Where they are made
  - Microfabrication unit (Specialized units)



How do they look like

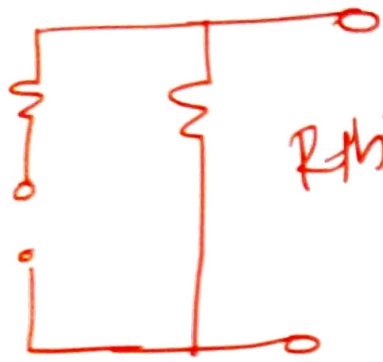

$$R_{th} = 1\Omega$$

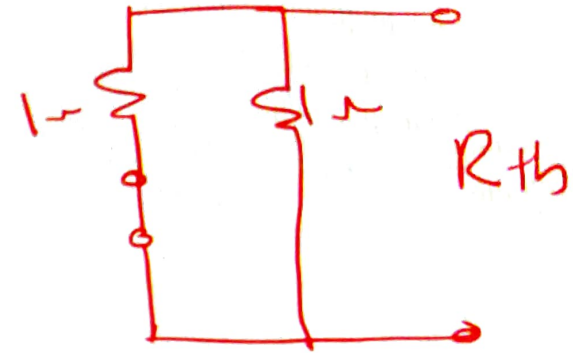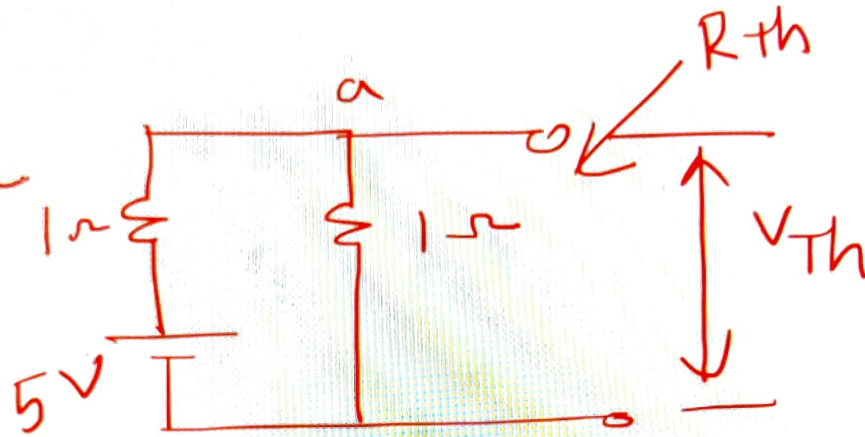

$$R_{th} = 0.5\Omega$$

