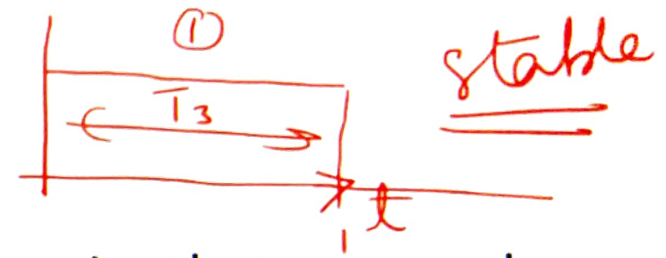


Multivibrators



- Multivibrators are a group of regenerative circuits that are used extensively in timing applications.
- They are wave shaping circuits which give symmetric or asymmetric square output.
- They have two states either stable or quasi-stable depending on the type of the multivibrator
 - Astable (free-running) ✓
 - Monostable (oneshot)
- All the three circuits operate by using positive feedback to drive the op-amp into saturation





Astable Multivibrator

- It is a free running oscillator
- It has two quasi-stable states, therefore oscillates between these two states
- External signal is **NOT** required to produce the change in state.
- The two states are stable only for a limited period of time and the circuit switches between them
- The output alternates between positive and negative saturation values



there is no external signal

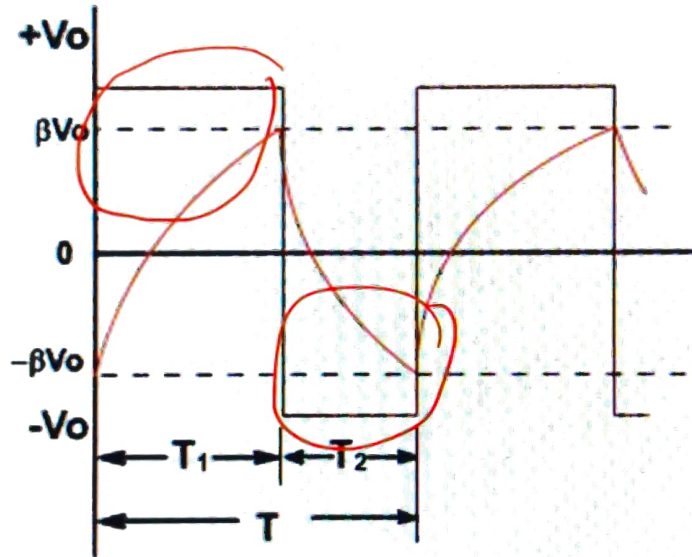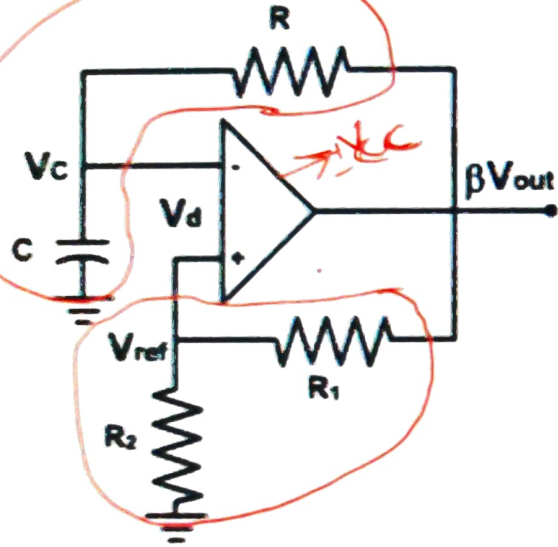Square wave generator (Astable multivibrator)



$$\beta = \frac{R_2}{R_1 + R_2}$$



Square wave generator (Astable multivibrator)

- Let, $v_o = +V_{sat}$

Voltage across the capacitor

$$v_c(t) = V_f + (V_i - V_f)e^{-t/RC}$$

Final value, $V_f = +V_{sat}$

Initial value, $V_i = -\beta V_{sat}$

$$\therefore v_c(t) = V_{sat} - V_{sat}(1 + \beta)e^{-t/RC}$$



At $t = T_1$

$$v_c(T_1) = \beta V_{sat}$$

$$\beta V_{sat} = V_{sat} - V_{sat}(1 + \beta)e^{-T_1/RC}$$

Solving
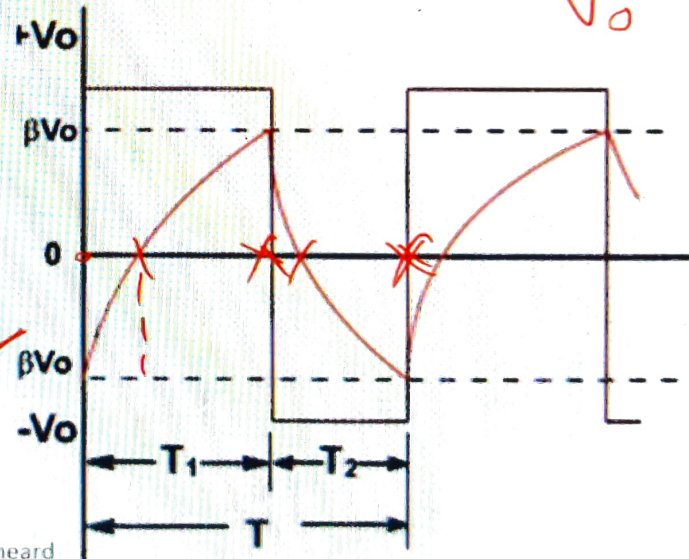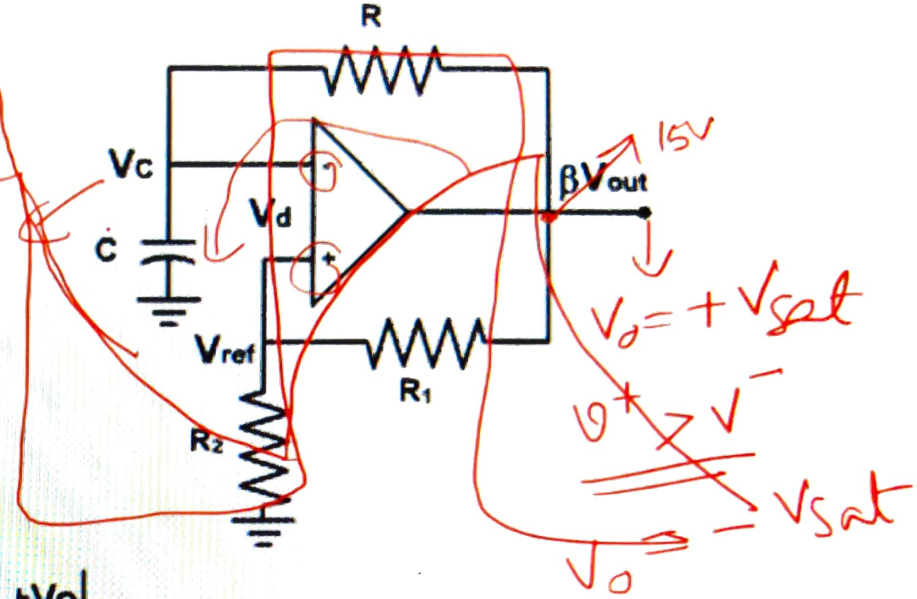
$$T_1 = RC \ln \left(\frac{1 + \beta}{1 - \beta} \right)$$




Monostable Multivibrator

- The circuit has one stable state and one quasi-stable state.
- The circuit remains in its stable state until an external triggering pulse causes a transition from stable state to the quasi-stable state.
- The circuit comes back to its stable state after a time period T .
- The circuit therefore generates a single output pulse in response to an input pulse and is referred to as a oneshot or single shot.
- An external trigger pulse is generated due to the charging and discharging of the capacitor.
- This trigger pulse produces the transition in the original stable state.
- MMV generates a single pulse of specified duration in response to each external trigger signal.




Monostable multivibrator

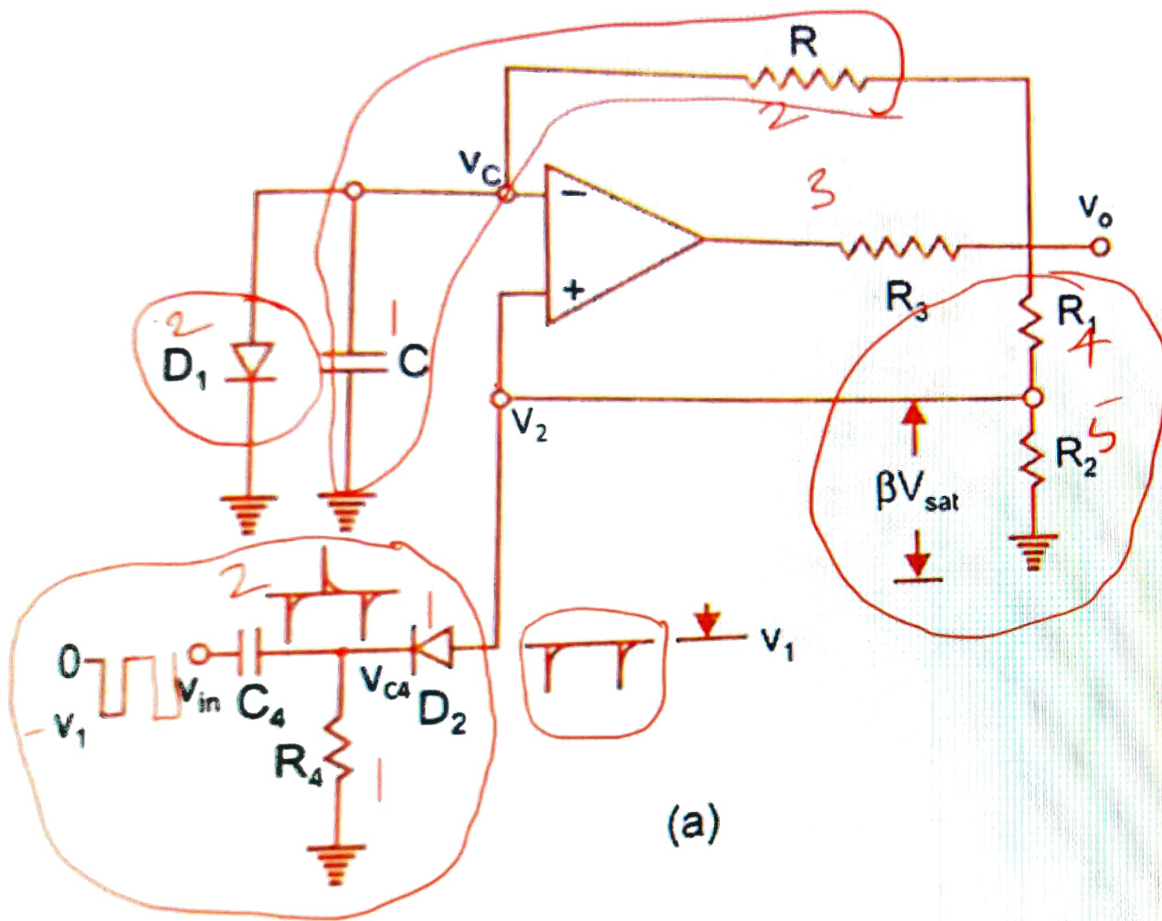

(a)

- Operational amplifier
- Two power supplies to the operational amplifier
- Resistors
- Two capacitors
- Two diodes

Monostable multivibrator

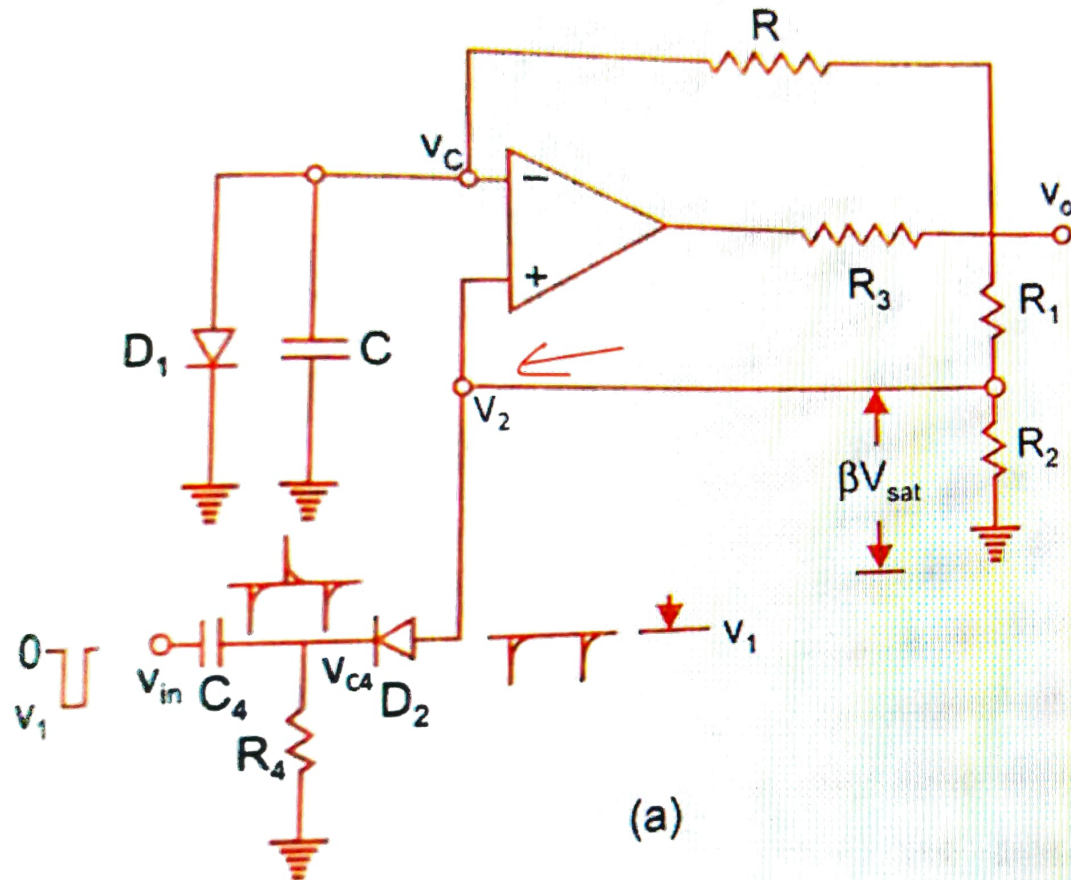


- Operational amplifier
- Two power supplies to the operational amplifier
- Resistors
- Two capacitors
- Two diodes

$$V_2 = \frac{R_2}{R_1 + R_2} V_o$$

$V_o \rightarrow +V_{sat}$
 $V_o \rightarrow -V_{sat}$

Monostable multivibrator

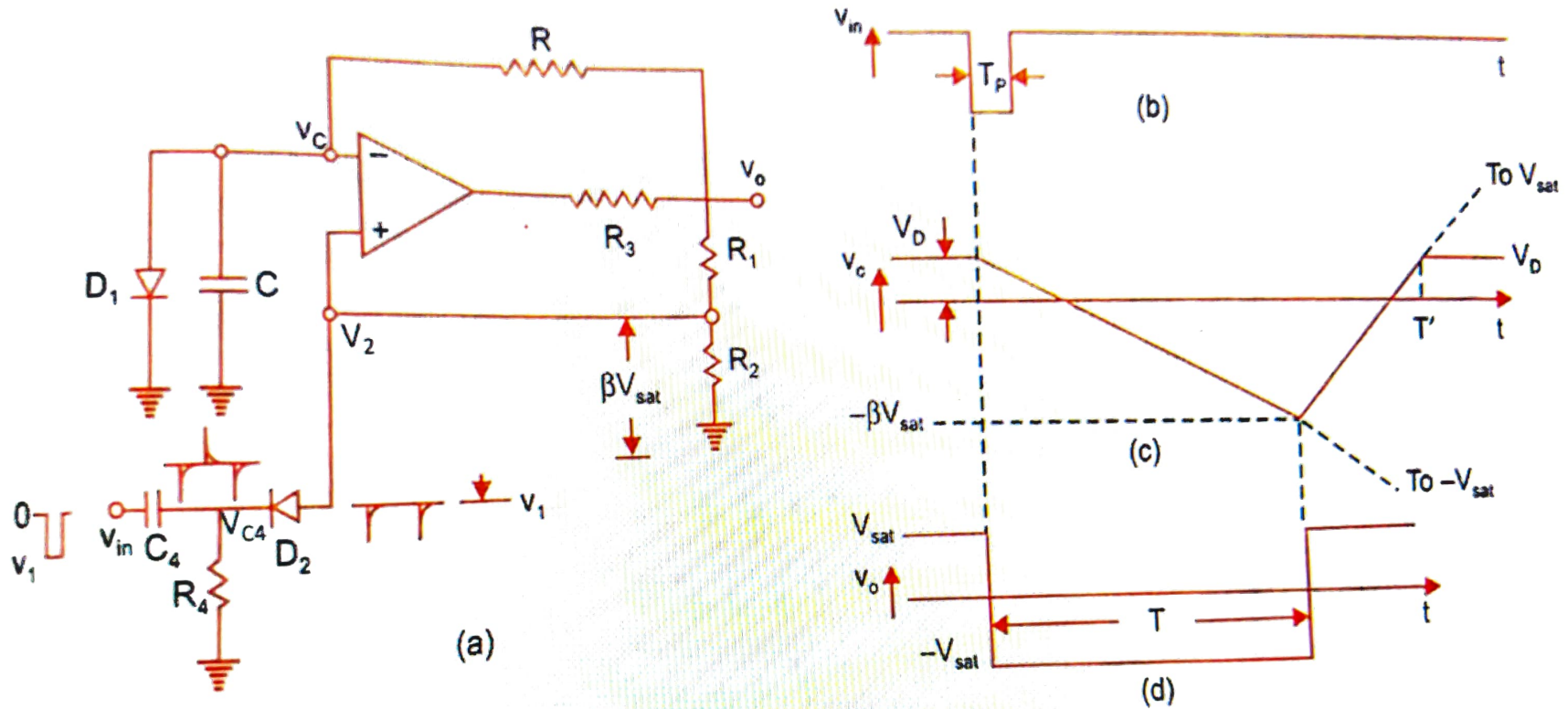

(a) Monostable multivibrator (b) Negative going triggering signal
(c) Capacitor waveform (d) Output voltage waveform

Monostable multivibrator

Voltage across the capacitor

$$v_c(t) = V_f + (V_i - V_f)e^{-t/RC}$$

Final value, $V_f = -V_{Sat}$

Initial value, $V_i = V_D$

$$\therefore v_c(t) = -V_{Sat} + (V_D + V_{Sat})e^{-t/RC}$$


At $t = T$

$$v_c(T) = -\beta V_{sat}$$


$$-\beta V_{sat} = -V_{Sat} + (V_D + V_{Sat})e^{-T/RC}$$

Solving
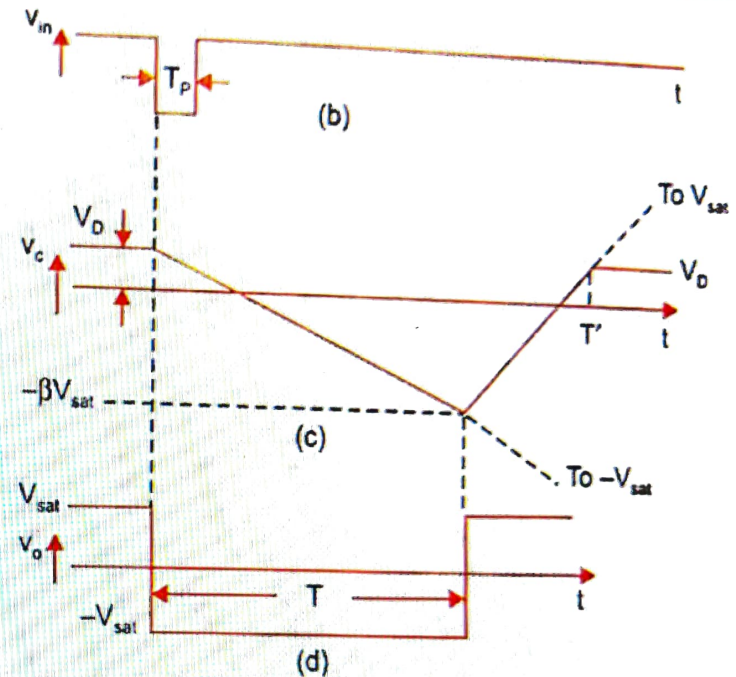
$$T = RC \ln \left(\frac{1 + \frac{V_D}{V_{Sat}}}{1 - \beta} \right)$$



$V_c \uparrow 0.71$
cut-ins

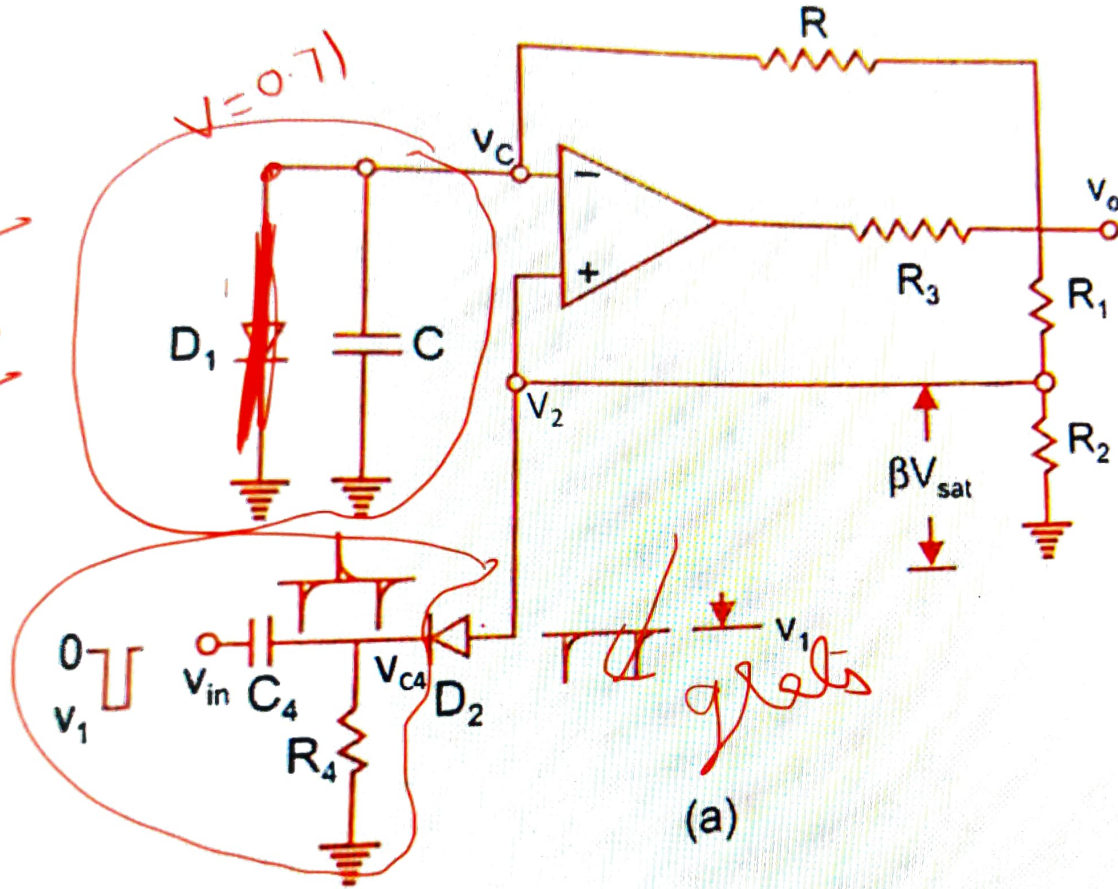

Monostable mult

Voltage across the capacitor

$$v_c(t) = V_f + (V_i - V_f)e^{-t/RC}$$

Final value, $V_f = -V_{Sat}$

Initial value, $V_i = V_D$

$$\therefore v_c(t) = -V_{Sat} + (V_D + V_{Sat})e^{-t/RC}$$

At $t = T$

$$v_c(T) = -\beta V_{sat}$$

$$-\beta V_{sat} = -V_{Sat} + (V_D + V_{Sat})e^{-T/RC}$$

Solving

$$T = RC \ln \left(\frac{1 + \frac{V_D}{V_{Sat}}}{1 - \beta} \right)$$

