

Low Pass Filter Example


A Low Pass Filter circuit consisting of a resistor of 4.7 kΩ in series with a capacitor of 47 nF is connected across a 10 V sinusoidal supply. Calculate the output voltage (V_{out}) at a frequency of 100 Hz, 200 Hz and again at frequency of 10kHz, 11 kHz.


$$X_c = \frac{1}{2\pi fC}$$

$$Z = R - jX_c$$

$$|Z| = \sqrt{R^2 + X_c^2}$$
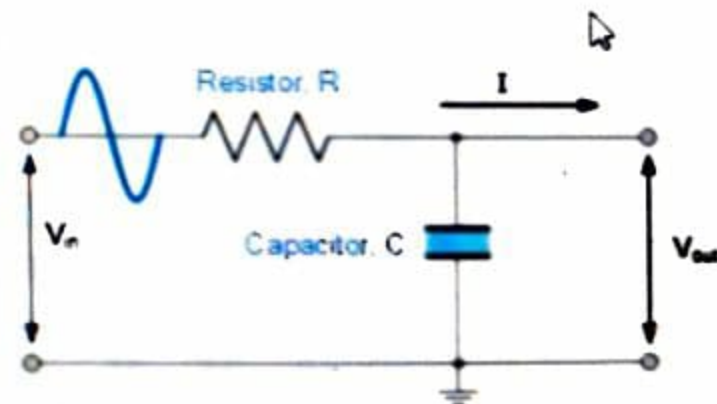
$$V_{out} = V_{in} \frac{X_c}{\sqrt{R^2 + X_c^2}} = V_{in} \frac{X_c}{Z}$$



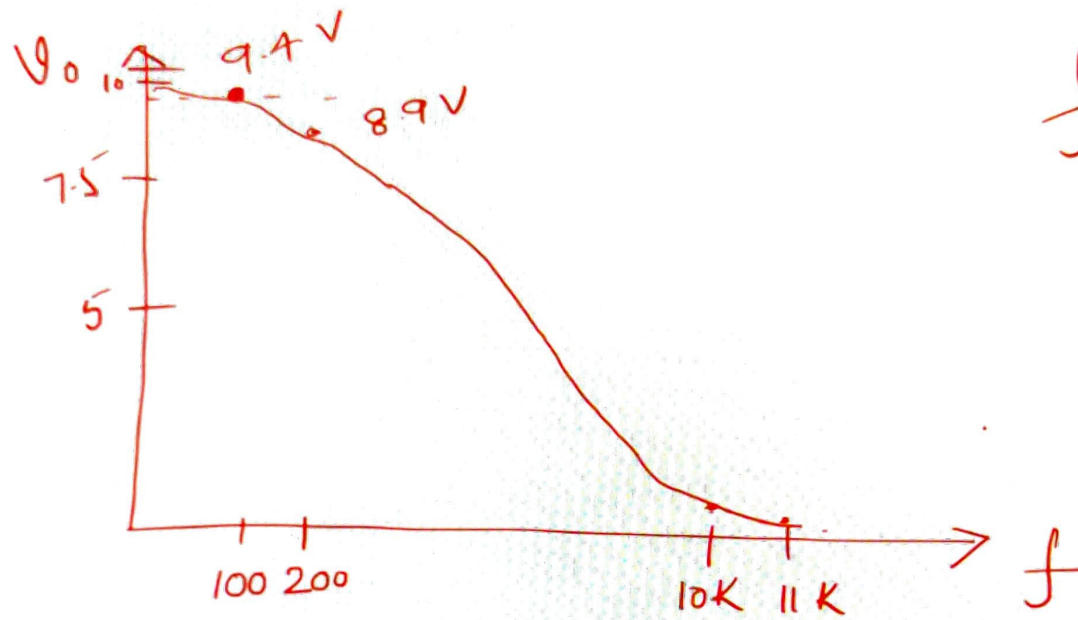

frequency
response
(V_o, f)

Low Pass Filter Example


A Low Pass Filter circuit consisting of a resistor of 4.7 kΩ in series with a capacitor of 47 nF is connected across a 10 V sinusoidal supply. Calculate the output voltage (V_{out}) at a frequency of 100 Hz, 200 Hz and again at frequency of 10kHz, 11 kHz.

$$X_c = \frac{1}{2\pi fC}$$

$$Z = R - jX_c$$

$$|Z| = \sqrt{R^2 + X_c^2}$$
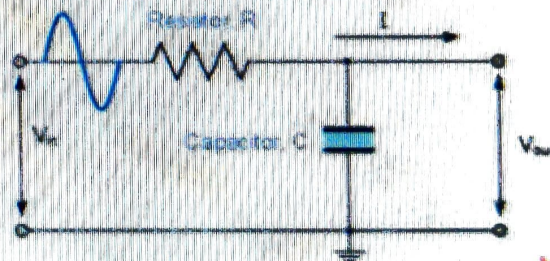
$$V_{out} = V_{in} \frac{X_c}{\sqrt{R^2 + X_c^2}} = V_{in} \frac{X_c}{Z}$$



$$X_c = 10\sqrt{47}$$


$$\begin{aligned} G &\rightarrow 100 \rightarrow \\ &\rightarrow 200 \text{ Hz} \rightarrow \\ &\rightarrow 10 \text{ kHz} \rightarrow \\ &\rightarrow 11 \text{ kHz} \rightarrow \end{aligned}$$

$$\frac{V_{in}}{\sqrt{\left(\frac{R}{X_c}\right)^2 + 1}}$$

$$= \frac{V_{in}}{\sqrt{1 + \left(\frac{RC}{2\pi f}\right)^2}}$$

$$\begin{aligned} X_c &= \frac{1}{2\pi fC} \\ 2\pi fC R &= \\ f_c &= \frac{1}{2\pi RC} \\ G &= \frac{1}{\sqrt{2}} \\ \frac{X_c}{\sqrt{R^2 + X_c^2}} &= \frac{1}{\sqrt{2}} \\ \frac{1}{\sqrt{\left(\frac{R}{X_c}\right)^2 + 1}} &= \frac{1}{\sqrt{2}} \\ \frac{R}{X_c} &= 1 \end{aligned}$$

Active filter

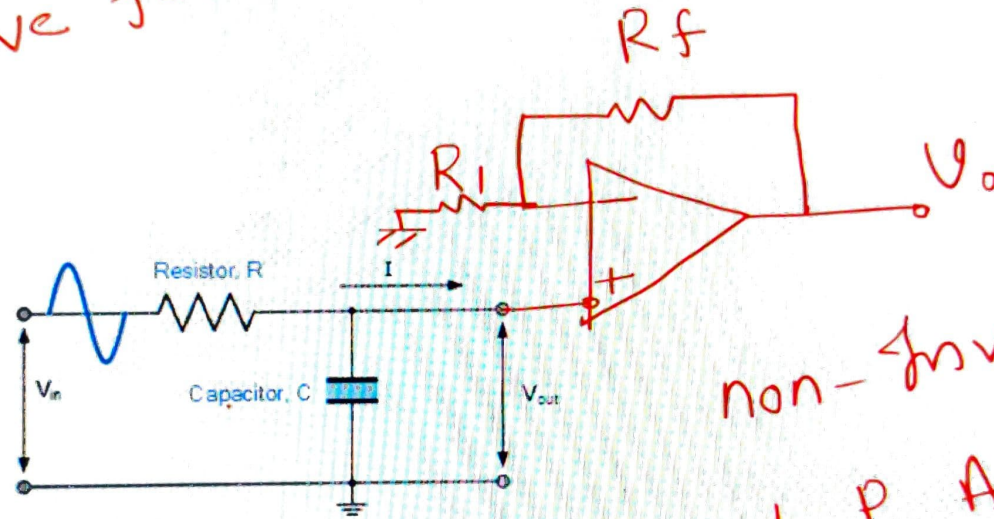

non-inverting
LP Active filter

non-inverting
HPAF
inverting
HPAF

←
Inverting
LP Active filter




High-pass RC filter

$$H(j\omega) = \frac{V_o}{V_i} = \frac{R}{R + 1/(j\omega C)} = \frac{1}{1 - j(1/\omega RC)}$$

gain
frequency response

when

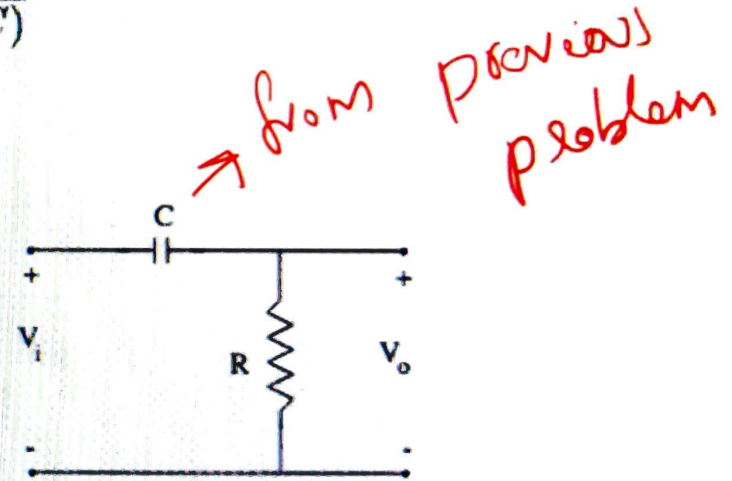$f = 100 \text{ Hz}$
 200 Hz
 10 kHz
 20 kHz





Start a business: \$999 - too much

Buy a new iPhone: \$999 - no problem

Healthy groceries: \$100 - too much

Dinner & drinks: \$100 - no problem

Watch Netflix: 2 hrs - 1 more episode



Learn a new skill: 2 hrs - no time

Life is about choices. stop blaming the


"LACK OF OPPORTUNITY."

clean
Gains
creative minds

frequency response of HPF

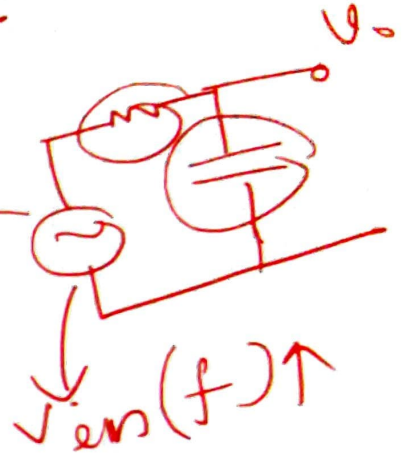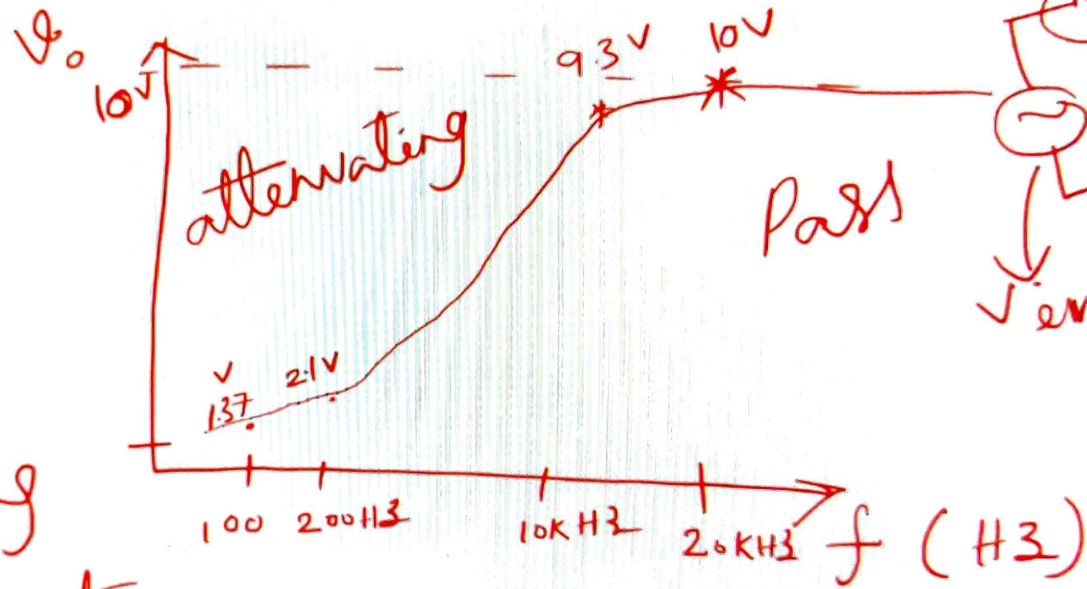


charging
fast

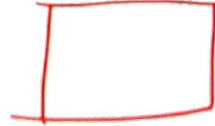


charging wire

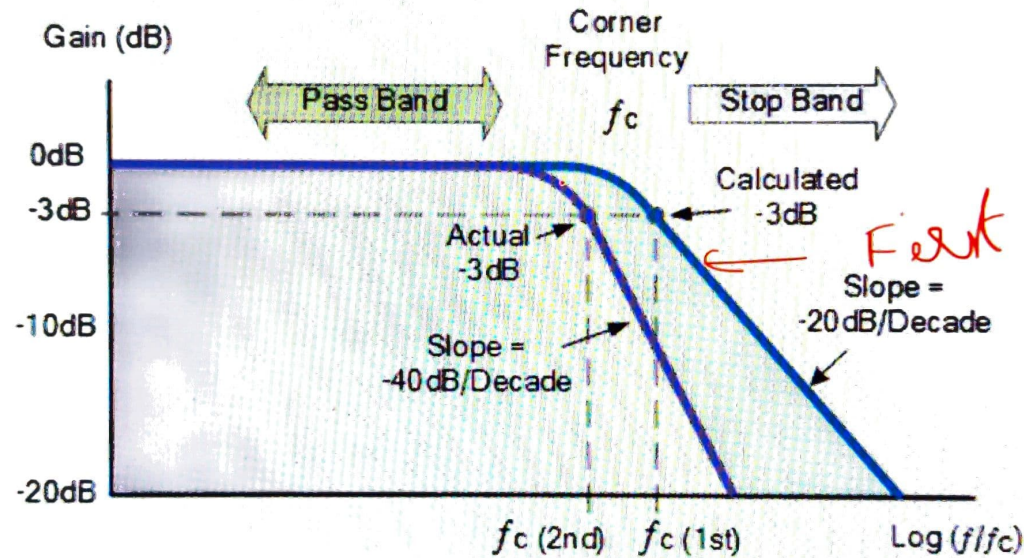Frequency Response of a 2nd-order Low Pass Filter




Second-order Low Pass Filter

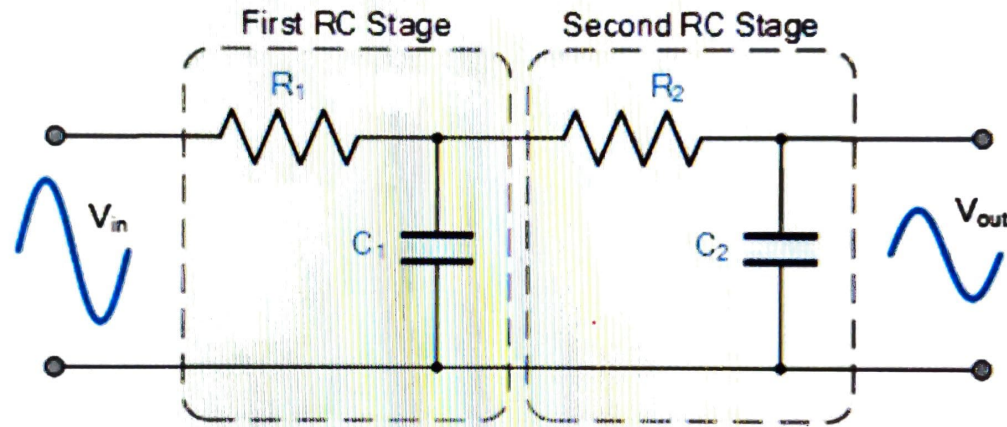


If -20dB/decade angle of the slope is not enough to remove an unwanted signal, then two stages of filtering can be used

The RC Integrator Circuit

*Simulate
in LT Spice*

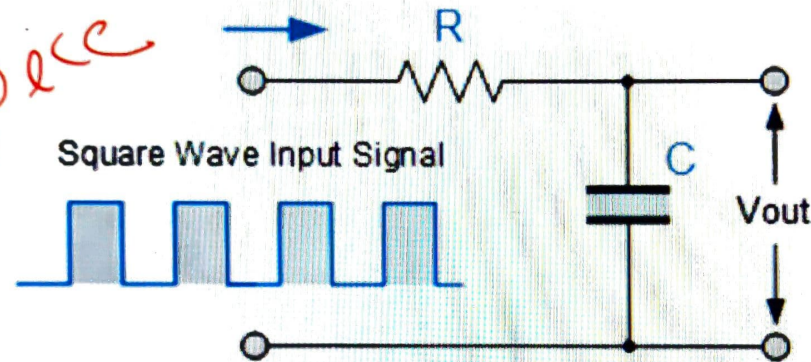

*Lab
hour*

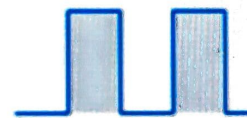

V_{out} at Low
Frequencies





V_{out} at Medium
Frequencies



V_{out} at High
Frequencies

First order low pass active filter

frequency response

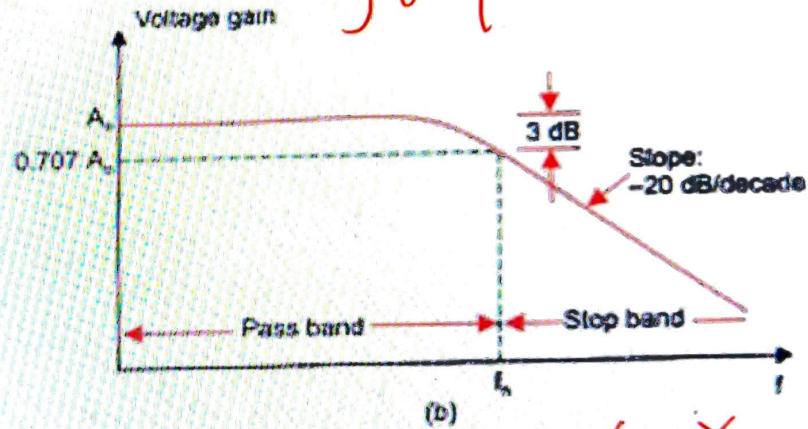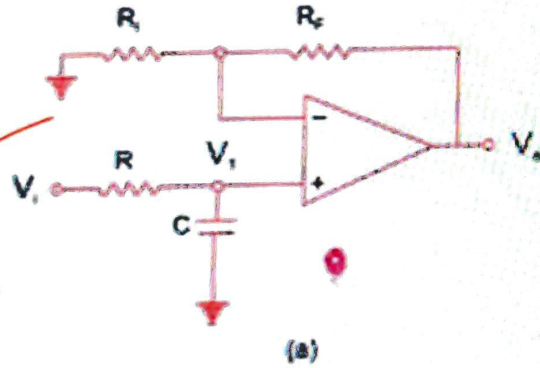

$$V_o = V_i \left(1 + \frac{R_F}{R_I} \right) \quad ; \quad V_i = V_i \left(\frac{-jX_C}{R - jX_C} \right)$$



Raise hand



Turn on captions



Paul Bra
is prese