

① SEVEN SEGMENT DISPLAY OF BCD NUMBERS


Aim:- To make segment display of BCD numbers

Software Used:- logism

Truth Table

INPUT				OUTPUT						
A	B	C	0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

logic diagram

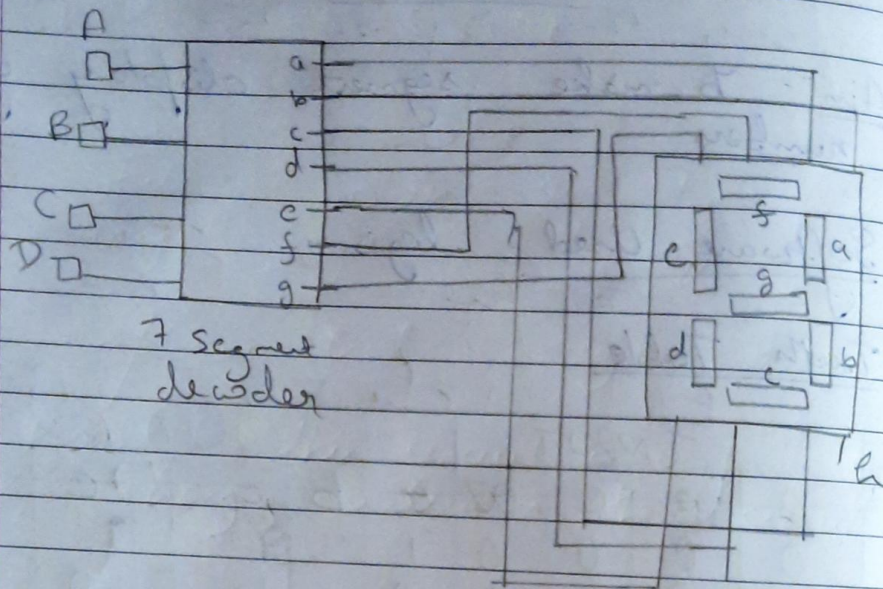

Conclusion:

The Seven Segment is simulated in logicism and is verified with inputs shown in above truth table

SEVEN SEGMENT DISPLAY OF HEXADECIMAL NUMBERS


AS n :- To make Seven Segment display of hexadecimal numbers.

Software used :- Logisim software

Truth Table :-

INPUT				OUTPUT						
A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

logic diagram

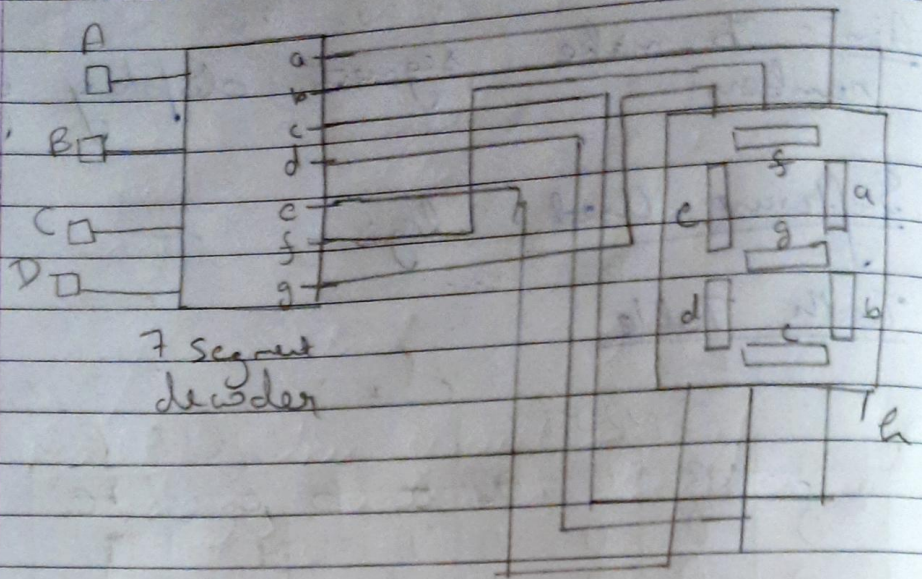

Conclusion:

The Seven Segment is simulated in logicism and is verified with inputs shown in above truth table

4-BIT FULL ADDER OUTPUT DISPLAY USING 7-BIT SEGMENT DISPLAY

Aim : To make 4-bit
Full adder output display
using 7 segment display

Software Used : Logisim Software

Result :- This circuit is verified by
changing values in the circuit

